

GUJARAT TECHNOLOGICAL UNIVERSITY**P.D.D.C. Sem- I Remedial Examination March / April 2010****Subject code: X11101****Date: 06 / 04 / 2010****Subject Name: Basic Electronics****Time: 12.00 noon – 02.30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw and explain the input and output characteristics of a CE transistor amplifier. **07**
- (b) State and prove Miller's theorem and its dual. **07**
- Q.2** (a) Prove that the transition capacitance for a step graded Junction diode is $C_T = EA/W$. **07**
- (b) Explain the following: (1) Hall effect (2) Reach-through In BJT. **07**
- OR**
- (b) Determine v_o for the network shown in **Figure 1** and **Figure 2**. **07**
- Q.3** (a) Explain fixed bias and self bias in a transistor. **07**
- (b) For the CE transistor amplifier, calculate various gains and input and output impedances for $R_L=10\text{ K}$ and $R_S=1\text{ K}$ with h parameters given below.
 $h_{ie} = 1100\ \Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 24\ \mu\text{A/V}$, $1/h_{oe} = 40\text{ K}$. **07**
- OR**
- Q.3** (a) Explain compensation techniques related with transistor biasing. **07**
- (b) Compare CB, CE and CC transistor configurations for A_i , A_v , R_i and R_o . **07**
- Q.4** (a) Draw the basic structure of an N channel FET and explain FET operation. **07**
- (b) Discuss transistor amplifier in a push-pull configuration. **07**
- OR**
- Q.4** (a) Discuss source self bias with respect to FET and FET as VVR. **07**
- (b) Define conversion efficiency. **02**
- (c) Explain crossover distortion and how to minimize it. **05**
- Q.5** (a) Explain the tunneling phenomenon and the V-I characteristics of a tunnel diode. **07**
- (b) A silicon transistor with $V_{BEsat} = 0.8\text{ V}$, $h_{FE}=100$ and $V_{CEsat} = 0.2\text{ V}$ is used in the circuit shown in **Figure 3**. Find the minimum value of R_c for which the transistor remains in saturation. **07**
- OR**
- Q.5** (a) For the emitter bias network shown in **Figure 4** determine the following **07**
 I_B , I_C , V_{CE} , V_C , V_E , V_B and V_{BC} , given $\beta = 50$.
- (b) Explain transistor as an amplifier. **07**

Figure 1.

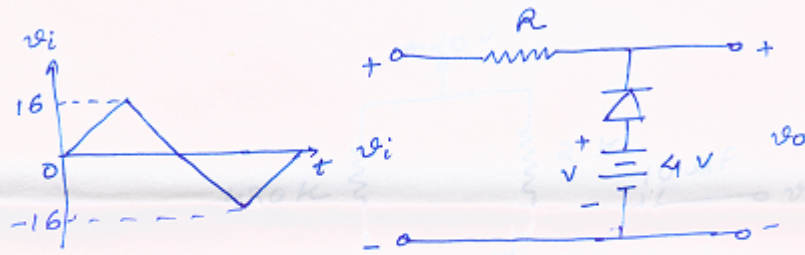


Figure 2.

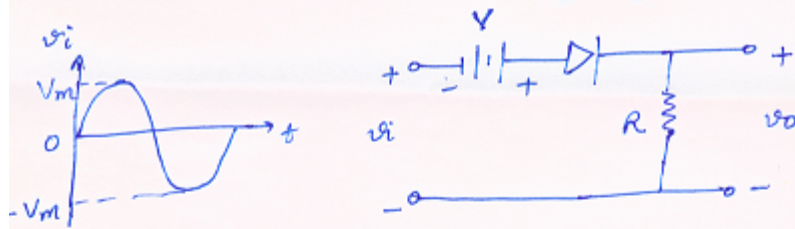


Figure 3.

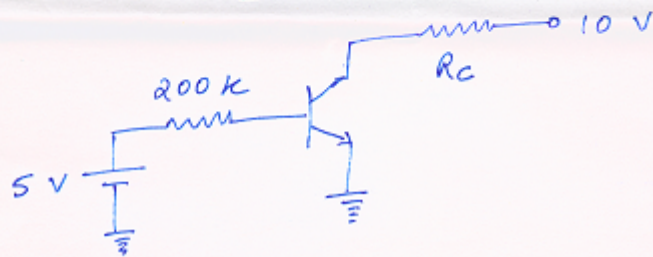


Figure 4

