

GUJARAT TECHNOLOGICAL UNIVERSITY**B. E. Semester-IV- Examination June- 2011****Subject code: 141101****Subject Name: Advance Electronics****Date: 08/06/2011****Time : 10:30 am to 1:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain working principal of colpitt's oscillator. Also derive the expression for frequency of oscillations. **07**
- (b) Write short note on Hybrid π model for a transistor in CE configuration and its circuit component. **07**

- Q.2** (a) What are the four possible topologies of feed back amplifier? Draw each with necessary details showing V_i , V_o , R_i , R_o , I_i , and I_o . Derive input and output resistance for each topology. **07**
- (b) Explain the working of RC coupled amplifier with neat diagram. Also obtain its frequency response. **07**

OR

- (b) Determine the voltage gain, input, and output impedance with feedback for voltage series feedback having $A = -100$, $R_i = 10 \text{ k}\Omega$, $R_o = 20 \text{ k}\Omega$ for feedback of (a) $\beta = -0.1$ (b) $\beta = -0.5$. **07**

- Q.3** (a) What is meant by differential amplifier ? And also explain the working of current source, with a circuit diagram. **07**
- (b) Determine output voltage of differential amplifier for input voltage of 300 μV & 240 μV . Differential gain is 5000 & CMRR is 100. **07**

OR

- Q.3** (a) Draw the circuit and explain the operation of transistorized Wien bridge oscillator. **07**
- (b) For Hartley oscillators $L_1 = 1\text{mH}$, $L_2 = 100 \mu\text{H}$, $m = 50 \mu\text{H}$, $C = 100 \text{ pF}$. Find its frequency. **07**

- Q.4** (a) Write short note on: Classification of amplifiers. **07**
- (b) Define following parameters. **07**
- I) Fan-out,
 - II) Propagation delay,
 - III) Speed power product,
 - IV) Slew rate,
 - V) CMRR,
 - VI) Gain bandwidth product,
 - VII) Power dissipation.

OR

- Q.4** (a) Using an OP-AMP, draw the functional diagram of a successive approximation ADC and explain its working. **07**

- (b) Explain transfer characteristics of differential amplifiers 07
- Q.5** (a) Write short note on: Validity of Hybrid – PI model. 07
- (b) Give the comparison between various logic families. 07
- OR**
- Q.5** (a) State Barkhausen in criteria for oscillation and Also explain stability criteria for sinusoidal oscillator. 07
- (b) Calculate the values of resistors and reference voltage if resolution required is 0.5 V for 4-bit R/2R ladder type DAC. 07
