

GUJARAT TECHNOLOGICAL UNIVERSITY**B.E. Sem-III Regular / Remedial Examination December 2010****Subject code: 130903****Subject Name: Electrical & Electronics Measuring Instruments****Date: 18 /12 /2010****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Define the following terms: **04**
 (1) Accuracy (2) Precision (3) Resolution (4) Drift
- (b)** The pull of an electromagnet is given by expression **05**
 $P \propto B^a A^b \mu_0^c$
 Where B = flux density in air gap
 A = area of electromagnets
 μ_0 = permeability of air gap
 Determine values of a, b, & c from the dimensions of quantities involved
- (c)** Explain errors in single phase energy meter **05**
- Q.2 (a)** Explain construction & working of a D' Arsonval Galvanometer **07**
(b) Draw the circuit diagram of a Crompton's Potentiometer & explain its working. **07**
 Describe the steps used when measuring an unknown resistance.
- OR**
- (b)** Explain construction & working of PMMC Instrument **07**
- Q.3 (a)** Give classification of analog instruments **06**
(b) Describe with a circuit diagram operation of an electronic voltmeter used in differential amplifier. **08**
- OR**
- Q.3 (a)** Explain briefly Weston Frequency Meter **06**
(b) Explain True RMS Reading Voltmeter **08**
- Q.4 (a)** Write short notes on following **14**
 (1) Absolute measurement of resistance (2) Maximum Demand Indicator
- OR**
- Q.4 (a)** Explain with a neat diagram working of a Synchroscope **07**
(b) Explain constructional details & working of an Electrodynamometer type 3-ph. p.f. meter **07**
- Q.5 (a)** Explain errors in Electrodynamometer type wattmeter **04**
(b) Explain how power can be measured in a 3- ph circuit with the help of two wattmeter **06**
(c) A 3-ph 500V motor load has a p.f of 0.4. Two wattmeters connected to measure the input. The input to be 30kW. Find the reading of each wattmeter **04**
- OR**
- Q.5 (a)** State advantages of Electronic Voltmeter over Conventional Voltmeter **04**
(b) Derive expression for Deflecting torque of a single phase induction type meter **05**
(c) In the measurement of power by a polar potentiometer the following readings were obtained **05**
 Voltage across a 0.2Ω standard resistance in series with the load = $1.46 \angle 32^\circ$.
 Voltage across a 200:1 potential divider across the line = $1.37 \angle 56^\circ$ V.
 Estimate the current, voltage, power & power factor of the load.
