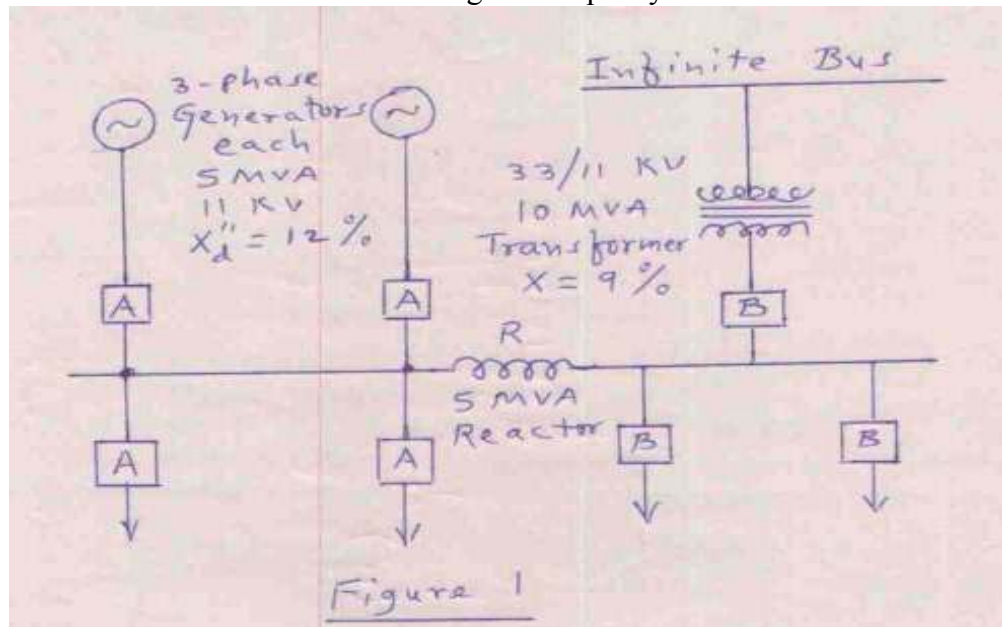


GUJARAT TECHNOLOGICAL UNIVERSITY**B.E. Sem-Vth Examination December 2010****Subject code: 150902****Subject Name: Power System Analysis and Simulation****Date: 15/12/2010****Time: 03.00 pm - 05.30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Using appropriate interconnection of sequence networks, derive the equation for a line to line fault in a power system with a fault impedance of Z_f . **07**
- (b)** Figure 1 shows a single-line diagram of power system network. The breaking capacity of breakers *A* is 100 MVA. Find out the per unit value of reactor *R*. Also find out the breaking capacity of breakers *B*. **07**



- Q.2 (a)** Figure 2 shows a power system network. Draw positive, negative and zero sequence networks. The system data is as under:

Equipment	MVA Rating	Voltage Rating	X_1	X_2	X_0
Gen. G_1	100	11 kV	0.25 p.u.	0.25 p.u.	0.05 p.u.
Gen. G_2	100	11 kV	0.2 p.u.	0.2 p.u.	0.05 p.u.
Transformer T_1	100	11/220 kV	0.06 p.u.	0.06 p.u.	0.06 p.u.
Transformer T_2	100	11/220 kV	0.07 p.u.	0.07 p.u.	0.07 p.u.
Line 1	100	220 kV	48.4 Ω	48.4 Ω	145.2 Ω
Line 2	100	220 kV	48.4 Ω	48.4 Ω	145.2 Ω

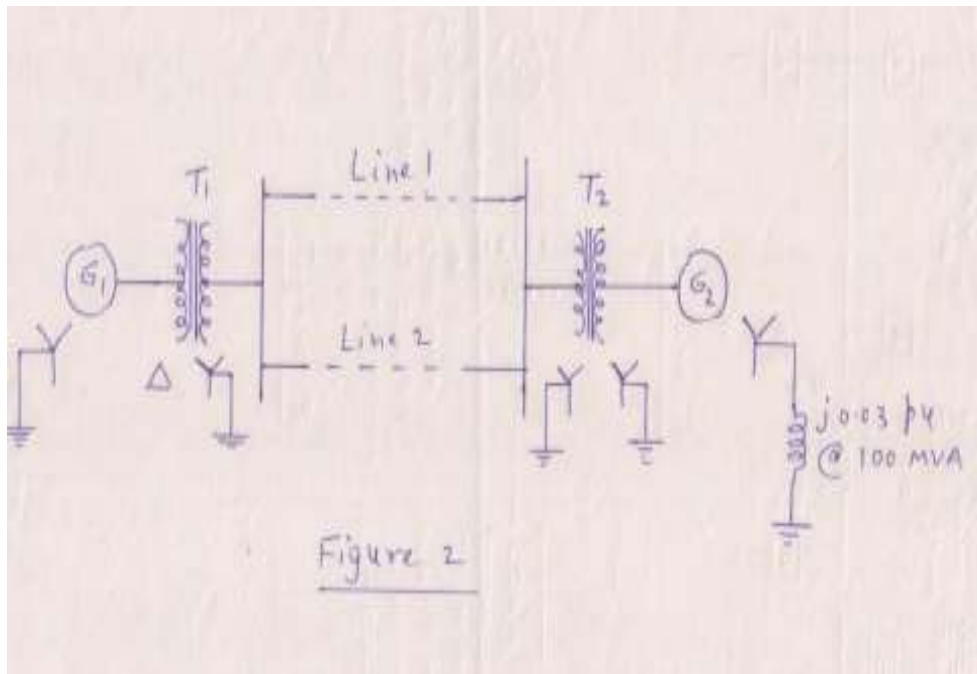


Figure 2

- (b) Two 25 MVA, 11 kV generators are connected to a common busbar which supplies a feeder. The star-point of one of the generators is grounded through a resistance of 1Ω , while that of the other generator is isolated. A line-to-ground fault occurs at the far end of the feeder. Determine: 07
- (i) the fault current and (ii) the voltage to ground of healthy phases of the feeder at the fault point. The sequence impedances of each generator and feeder are given below:

	Each Generator (p.u.)	Feeder ($\Omega/\text{ph.}$)
X_1	$j 0.2$	$j 0.4$
X_2	$j 0.15$	$j 0.4$
X_0	$j 0.08$	$j 0.8$

Assume fault impedance to be zero.

OR

- (b) A 25 MVA, 11 kV generator has $X_d'' = 0.2$ p.u., $X_2 = 0.3$ p.u. and $X_0 = 0.1$ p.u.. 07
- The neutral of the generator is solidly grounded. Determine the sub-transient current in the generator and the line-to-line voltages for sub-transient condition when a Y-B-G fault occurs at the generator terminals. Assume pre-fault currents and fault-resistance to be zero.

- Q.3 (a) From first principles, derive the A, B, C and D constants of a long transmission line. 07
- (b) A long line with $A = D = 0.9 \angle 1.5^\circ$ and $B = 150 \angle 65^\circ$ has at the load end, a transformer having a series impedance $Z_T = 100 \angle 67^\circ$. The load voltage and current are V_L and I_L . Obtain expressions for V_S and I_S in the form: 07

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_L \\ I_L \end{bmatrix} \text{ and evaluate these constants.}$$

OR


- Q.3 (a) Prove that the active and reactive powers transmitted to load over a long line are 07
- given by $P_R = \frac{V_S V_R}{X} \sin \delta$ and

$$Q_R = \frac{V_S V_R}{X} \cos \delta - \frac{V_R^2}{X}.$$

- (b) A short 230 kV transmission line with a reactance of $18 \Omega/\text{ph}$ supplies a load at 0.85 p.f. lag. For a line current of 1000 A, the receiving and sending end voltages are to be maintained at 230 kV. Calculate: (i) rating of synchronous capacitor required (ii) load current (iii) load MVA. Neglect power drawn by the capacitor. **07**

Q.4 (a) Discuss the advantages of per unit computations. **07**

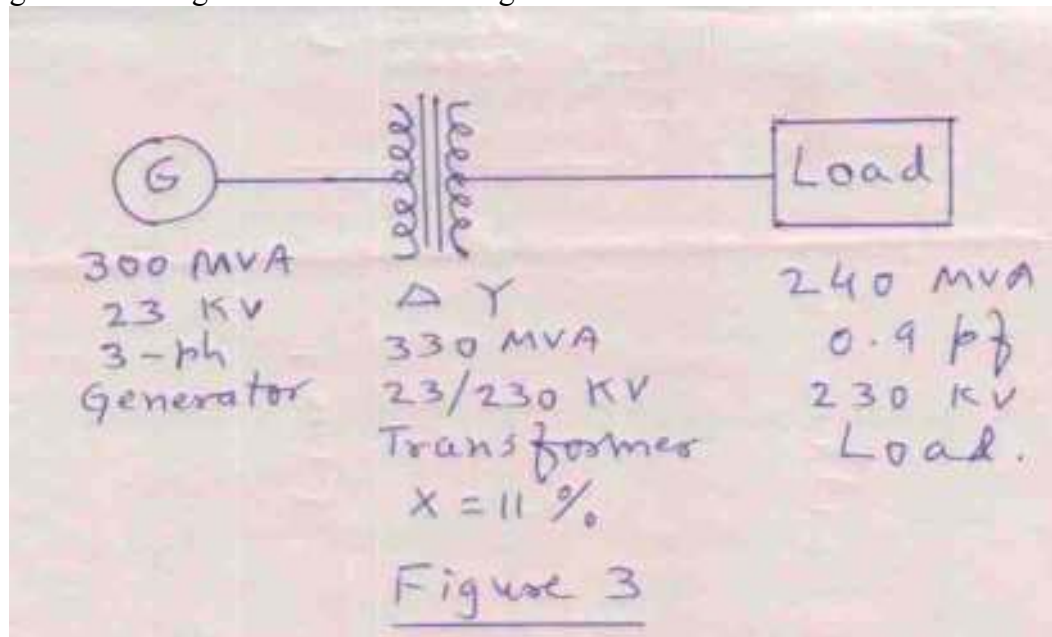- (b) Figure 3 shows a three phase generator rated 300 MVA, 23 kV. It supplies a system load of 240 MVA, 0.9 p.f. lag at 230 kV through a 330 MVA, 23/230 kV DY step-up transformer of leakage reactance 11 %. Neglecting magnetizing current and choosing base values at the load as 100 MVA and 230 kV, find currents I_A , I_B and I_C supplied to the load in p.u. with V_A (voltage of h.v. side for A phase) as reference. Also determine currents I_a , I_b and I_c supplied by the generator and generator terminal voltage. **07**



OR

Q.4 (a) What are the factors and conditions affecting corona loss? Explain them briefly. **07**

- (b) Find the disruptive critical voltage for a 3-ph line consisting of 21 mm diameter conductors spaced in a 6 m delta configuration. Take temperature as 25°C , pressure as 73 cm of Hg and surface factor 0.85. What should be the voltage of transmission? **07**

Q.5 (a) Explain different systems of neutral grounding and compare them. **07**

- (b) Starting from the first principles, show that surges behave as travelling waves. Find expressions for surge impedance and wave velocity. **07**

OR

Q.5 (a) Draw the waveforms for fault current for a 3-phase fault on alternator terminals. Explain the sub-transient, transient and steady state reactance. What is their significance in fault calculations? **07**

- (b) Justify the following statement: "For a fault at alternator terminals, a single line to ground fault is generally more severe than a 3-ph fault whereas for faults on transmission lines, a 3-ph fault is more severe than other faults." **07**
