

GUJARAT TECHNOLOGICAL UNIVERSITY**B.E. Sem-Vth Examination December 2010****Subject code: 152403****Subject Name: Applied Power Electronics****Date: 16 /12 /2010****Time: 03.00 pm - 05.30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) State various Application areas of Power Electronics. Also list out various applications of Power Electronics in these areas. **07**
- (b) What is 'Signal Processing'? What are different functions of signal processing? What is importance of signal processing in Power Electronics? **07**
- Q.2** (a) Explain working of following circuits with neat schematic diagram. Derive input-output relationship. **07**
- a. Difference Amplifier b. Log Amplifier
- (b) Explain working principle of Switched Capacitor Circuit. Draw schematic diagram of switch capacitor realization of resistance. Using switched capacitor circuit, implement inverting amplifier. **07**
- OR**
- (b) State various types of Analog to Digital Converters. Explain dual slope integration type ADC with necessary waveforms and schematic diagram. State at least one ADC. **07**
- Q.3** (a) What is a Filter Circuit? What are different Types of Filter Circuits? Draw frequency responses of various filter circuits. **07**
- (b) What is PWM? Draw block diagram and explain working of PWM generator. State importance of PWM in Power Processing Circuits. **07**
- OR**
- Q.3** (a) What is PLL? Explain working principle of PLL with neat diagram. State various applications of PLL. Name any one IC chip which can be used in PLL circuit. **07**
- (b) Draw schematic diagram of state variable filter. Explain working of the same. **07**
- Q.4** (a) Explain principle of Phase control. With neat diagram explain working of 1- ϕ Controlled rectifier. **07**
- (b) What is a Motor Drive? Explain with neat diagram. State types of Motor Drives. **07**
- OR**
- Q.4** (a) What is Chopper? Explain basic DC chopper circuit. State types of chopper and explain. **07**
- (b) With neat block diagram explain working of speed control of separately excited DC Motor using solid state components. **07**
- Q.5** (a) State types of SMPS. Explain with neat diagram working of buck converter. **07**
- (b) What is UPS? Why it is required? State types of UPS. Draw block diagram and explain working of on Line UPS. **07**
- OR**
- Q.5** (a) With neat diagram explain working principle of **07**
- (1) high frequency fluorescent lighting
- (2) Induction Heating
- (b) What is Simulation? Explain its importance in Power Electronics. **07**
