

GUJARAT TECHNOLOGICAL UNIVERSITY
BE SEM-III Examination-Dec.-2011

Subject code: 131901**Date: 20/12/2011****Subject Name: Electrical Machines & Electronics****Time: 2.30 pm -5.00 pm****Total marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw circuit diagrams of different types of D.C.generators. **07**
Write current & voltage equations for each
- (b) Explain the construction features and working principle of a single phase transformer **07**

- Q.2** (a) Why Starters are used in d.c.shunt motors? Explain 3-point Starter With neat diagram **07**
- (b) A long shunt generator running at 1200 r.p.m. supplies 22 KW at a terminal voltage of 220 V .The resistances of armature, shunt field and the series field are 0.05,110 and 0.06 Ω respectively. The overall efficiency at above load is 88%. Find (1) Cu losses (2) Iron &friction losses (3) The torque exerted by the prime mover. **07**

OR

- (b) A 100 KW (output),3300-V,50 Hz,3phase ,star connected induction motor has a synchronous speed of 500 r.p.m .The Full load slip is 1.8% and full load power factor 0.85.Stator copper loss 2440 W, Iron loss 3500 W. Rotational loss 1200 W. Calculate **07**
(1) The rotor copper loss (2) The line current (3) The full load Efficiency

- Q.3** (a) Derive condition for maximum torque for induction motor and explain Torque-Slip and Torque- speed characteristics. **07**
- (b) What is Voltage Regulation of an alternator ?Explain Synchronous Impendence Method **07**

OR

- Q.3** (a) Why Single phase induction motor is not self starting motor? Explain double field revolving theory for the same motor. **07**
- (b) Explain different methods of speed control of three phase induction motor. **07**

- Q.4** (a) Comparison between A.C & D.C Transmission. **07**
- (b) What do you mean by Tariff? Explain different types of Tariff. **07**

OR

- Q.4** (a) Discuss the disadvantages of a low power factor. Also explain the methods of power factor improvement. **07**
- (b) Write the name of equipment used in a substation with Symbols **04**

- (c) Find the most economical power factor ,when the tariff is Rs 100/- per KVA of maximum demand plus a flat rate per KWh. Assume additional cost of condenser of Rs 80/- per KVA. Rate of interest & depreciation is together to be taken as 10 % **03**
- Q.5** (a) What is Rectification? With the help of neat circuit diagram & wave form explain the operation of a centre tapped full wave rectifier. **07**
- (b) Explain single stage CE amplifier with neat circuit diagram **04**
- (c) State Ideal characteristics of an OP-AMP **03**
- OR**
- Q.5** (a) What is Logic-Gate ?Draw the Truth table & symbol for NAND, NOR, OR Gate. Also State & Explain De-Morgan's Theorem. **07**
- (b) Draw & Explain Internal architecture of 8085 microprocessor. **07**
