

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

B. E. Vth Semester–Examination – Nov-Dec- 2011

Subject code: 152401

Subject Name: Power Electronics Devices and Instruments.

Date: 22/11/2011

Time: 02:30 pm – 05:30 pm

Total Marks: 70

Instructions:

- 1. Attempt all questions.**
- 2. Make suitable assumptions wherever necessary.**
- 3. Figures to the right indicate full marks.**

- Q.1** (a) Explain Power Electronics system with block diagram. **07**
(b) Discuss the ideal switch characteristics. Why does power loss take place in practical switch? **07**
- Q.2** (a) Explain opto-coupler. **07**
(b) Explain UJT based relaxation oscillator circuit with neat diagram. Also derive an expression for oscillating frequency of relaxation oscillator. **07**
- OR**
- (b) Discuss behavior of inductor and capacitor at different frequencies. **07**
- Q.3** (a) Explain Schottky barrier diode. **07**
(b) What is PiN diode? Discuss with forward, reverse and switching characteristic. **07**
- OR**
- Q.3** (a) Explain structure and working of power BJT. **07**
(b) Discuss driving circuit for power BJT used as a switch. **07**
- Q.4** (a) Explain two transistor analogy of SCR. Also give its characteristics indicating its mode of operation. **07**
(b) Explain snubber circuit for SCR. **07**
- OR**
- Q.4** (a) What is commutation of SCR? Explain Class B commutation circuit. **07**
(b) Discuss Thyristor specification/ratings in brief. **07**
- Q.5** (a) Discuss switching characteristic of Power MOSFET with necessary waveforms. **07**
(b) Explain construction and working of IGBT. **07**
- OR**
- Q.5** (a) Explain TRIAC. Also draw its characteristics. **07**
(b) Explain working of MCT with neat diagram. **07**
