

GUJARAT TECHNOLOGICAL UNIVERSITY**B. E. Vth Semester–Examination – Nov-Dec- 2011****Subject code: 152402****Subject Name: Electrical Measurements & Electronics Instruments****Date: 24/11/2011****Time: 02:30 pm – 05:30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw the equivalent circuit and Phasor diagram of a current transformer. Drive the expression for ratio and phase angle errors. **07**
- (b) Define following terms :- **07**
- 1) Repeatability, 2) Accuracy, 3) Precision,
 - 4) Resolution, 5) Linearity, 6) Johnson Noise,
 - 7) White noise.

- Q.2** (a) Explain the principle and operation of d'Arsonval galvanometer. **07**
- (b) Describe in detail the successive approximation method of analog to digital (A/D) conversion. **07**

OR

- (b) Discuss the measurement of Power in a 3-phase circuit by two watt-meter method with neat diagrams. **07**

- Q.3** (a) Differentiate Attraction type and Repulsion type Moving Iron instruments. **07**
- (b) Calculate the inductance of a coil from the following measurement on an a.c. potentiometer. **07**
- 1) Voltage drop across a 0.1Ω standard resistor connected in series with the coil = $0.613 \angle 12^\circ 6'$
 - 2) Voltage across the test coil through a 100/1 volt-ratio box = $0.781 \angle 50^\circ 48' V$.
 - 3) Frequency is 50 Hz.

OR

- Q.3** (a) Sketch the circuit diagram of a Maxwell bridge. Drive the equations for the resistive and inductive components of the measured inductor. **07**
- (b) The constant for a 3-phase 3 element integrating wattmeter is 0.12 revolution of disc/kwh. If the meter is normally used with a potential transformer of a ratio 12000/110V and a current transformer of ratio 500/5A, find the error expressed as a percentage of the correct reading from the following test figures for the instrument only. **07**
- 1) Line voltage = 100V
 - 2) Current = 5.25A
 - 3) Power factor = 1
 - 4) Time to complete 40 revolutions = 61 sec.

- Q.4** (a) Describe the construction and working of PMMC instruments. **07**
- (b) Explain the constructional details and working of Ferro-dynamic watt meters. Enlist advantages and disadvantages of same. **07**

OR

- Q.4** (a) Sketch the complete circuit of an emitter follower voltmeter using a FET input stage. Carefully explain the circuit operation and the effect of the FET. **07**

- (b) Briefly describe a thermocouple. Draw a sketch to show the construction of a basic thermocouple instruments. Explain its operation. **07**
- Q.5** (a) Sketch a range changing circuit for a Digital Volt Meter & explain how it operates. **07**
- (b) Explain the source of errors in 1-phase induction type energy meters. **07**
- OR**
- Q.5** (a) Draw basic block diagram of a digital frequency meter. Discuss each block in details. **07**
- (b) Enlist various types of Probes. Explain any two in detail. **07**
