

GUJARAT TECHNOLOGICAL UNIVERSITY**B. E. Vth Semester–Examination – Nov-Dec- 2011****Subject code: 152403****Subject Name: Applied Power Electronics****Date: 26/11/2011****Time: 02:30 pm – 05:00 pm****Total Marks:****70 Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations/symbols used have usual meanings.

Q.1 (a) Draw astable multivibrator using IC 555. Determine the frequency and duty cycle for the IC 555 astable multivibrator output for $C=0.01\mu F$, $R_A=2K\Omega$ and $R_B=100K\Omega$. **07**

(b) Describe R-2R ladder network for analog to digital conversion. **07**

Q.2 (a) Define PLL. Explain operation of PLL using block diagram. State its applications. **07**

(b) Draw and explain 1st order low-pass filter using necessary diagrams. **07**

OR

(b) Define power electronics. State its requirements and enlist various application areas of the power electronics field. **07**

Q.3 (a) With the help of basic power diagram, explain working of an inverter. Where inverter circuits are used practically? **07**

(b) Define filter. Describe state variable filter with necessary diagrams. **07**

OR

Q.3 (a) Write a detailed note on :- HVDC Transmission. **07**

(b) What is Pulse Width Modulation? Explain pulse width modulator using necessary diagram and waveforms. **07**

Q.4 (a) Classify methods of heating. Explain the principal of Induction Heating. **07**

(b) Describe with block diagram SMPS. State difference between SMPS and UPS, also. **07**

OR

Q.4 (a) Discuss the applications of ultrasonic as (i) soldering (ii) cutting of hard materials. **07**

(b) With neat diagram, explain construction and working of a battery. **07**

Q.5 (a) Discuss working principle of DC motor drives in detail. **07**

(b) Write short note on:- Air- Conditioning System. **07**

OR

Q.5 (a) Enlist applications of motor drive and explain any two of them in detail. **07**

(b) Discuss the concept of simulation of Power Electronics System. **07**
