

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE SEM-VI Examination-Nov/Dec-2011

Subject code: 162405

Date: 30/11/2011

Subject Name: Power Processing Circuits-I

Time: 10.30 am -1.00 pm

Total marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations used have usual meaning.

- Q.1** (a) Explain operation of single phase semi converter with R-L load. Also draw necessary waveforms. **07**
(b) Compare single phase and three phase rectifier circuits. **07**
- Q.2** (a) Explain single phase full bridge uncontrolled rectifier with neat sketch. Draw appropriate waveforms. **07**
(b) Discuss the effect of source inductance on converter operation. **07**
- OR**
- (b) Explain inverter mode control of controlled rectifier. **07**
- Q.3** (a) Draw and explain basic block diagram of linear regulated power supply. **07**
(b) Explain class A chopper circuit and deduce an expression for output voltage of chopper circuit. **07**
- OR**
- Q.3** (a) Discuss IC based 78xx positive voltage regulator. **07**
(b) Draw and explain jone's chopper circuit with neat diagram. **07**
- Q.4** (a) Explain working of class B chopper circuit neat diagram. **07**
(b) A step down chopper is supplied through Vdc feeding to resistive load. Find an expression for (i) average output voltage (ii) rms output voltage (iii) input resistance to chopper circuit. **07**
- OR**
- Q.4** (a) A resistive load R is fed through single phase half wave controlled rectifier. Find an expression for (i) average output voltage (ii) rms output voltage **07**
(b) Explain concept of resonant based ZCS converter in brief. **07**
- Q.5** (a) Draw and explain three phase half wave rectifier circuit with neat diagram. **07**
(b) Explain working of SEPIC DC to DC converter circuit. **07**
- OR**
- Q.5** (a) Discuss fly-back DC to DC converter. **07**
(b) Explain multi phase chopper circuit with necessary waveforms. **07**
