

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- VIIth SEMESTER-EXAMINATION – MAY/JUNE- 2012****Subject code: 172401****Date: 24/05/2012****Subject Name: Power Electronics Systems Modelling****Time: 02:30 pm – 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Define modeling. Draw and Explain the block diagram of Power Electronics System with reference to modeling. **07**
- (b) State inductor voltage-second balance principle and explain its use in buck converter. **07**

- Q.2** (a) Explain the concept of controllability and observability of the system. Find the complete state controllability of a converter whose state-space equation

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} u$$

- (b) Explain the modeling the boost converter inclusion inductor copper loss. Draw the waveform for inductor voltage and capacitor current waveforms. **07**

OR

- (b) Explain the modeling of the boost converter inclusion of semiconductor conduction losses. Draw the waveform for inductor voltage and capacitor current. **07**

- Q.3** (a) Explain the working of the CUK converter with neat circuit diagram and necessary waveforms. Explain the graph for DC conversion ratio $M(D)$ with duty cycle. **07**
- (b) For buck converter following data given are: Input voltage = 48 V, Mark Space Ratio = 0.25, Switching Frequency = 100 KHz, Load Resistance = 6 Ω . Determine V_o and I . Calculate the value of L that will make the peak inductor current ripple ΔI equal to 10 % of the average inductor current I . **07**

OR

- Q.3** (a) Explain working of open loop control with feedforward for an up/down converter with necessary circuit and waveform. **07**
- (b) For boost converter following data given are: Input voltage = 12 V, Mark Space Ratio = 0.75, Switching Frequency = 100 KHz, Load Resistance = 8 Ω . Determine V_o and I . Design the value of C such that peak output voltage ripple ΔV is 0.1 V_o . **07**

- Q.4** (a) Explain the basic AC modeling approach using buck boost converter example and draw the average inductor voltage and inductor current waveform. **07**
- (b) Develop state space model of basic buck converter. **07**

OR

- Q.4** (a) What is canonical circuit model? Explain the development of canonical circuit model based on physical arguments. **07**
- (b) Develop state space model of buck boost converter. **07**

- Q.5** (a) Derive and plot the control-to-output transfer function for circuit of small signal equivalent circuit model of buck boost converter. **07**
- (b) Draw and explain the modeling of PWM. **07**

OR

- Q.5** (a) Derive and plot the line-to-output transfer function for circuit of small signal equivalent circuit model of buck boost converter. **07**
- (b) Derive the transfer function for armature controlled DC Motor and develop block diagram for the same. **07**
