

GUJARAT TECHNOLOGICAL UNIVERSITY**BE SEM-VIII Examination May 2012****Subject code: 180907****Subject Name: Advanced Power Electronics II (Department Elective-II)****Date: 08/05/2012****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) State the advantages HVDC transmission over EHVAC transmission for bulk power transmission. **07**
- (b) Obtain the relation between the output voltage and the AC line voltage (rms) and expression for PIV and peak-to-peak ripple of the converter transformer with Graetz's converter circuit. **07**

- Q.2** (a) Compare the performance of EHVAC link with HVDC link for (i) same insulation level and (ii) same power transmitted. **07**
- (b) Derive the equations for power flow in an HVDC link. How are the losses estimated? **07**

OR

- (b) What is an HVDC-VSC system? Give the single line diagram of the system. **07**

- Q.3** (a) What is extinction angle control? What are its limitations under asymmetrical fault? **07**
- (b) Give comparison between CSC (Classical HVDC) and HVDC-VSC systems. **07**

OR

- Q.3** (a) Explain working of TCR. Draw waveforms of voltage and current for different values of α . **07**
- (b) Explain the necessity of compounding both rectifier and inverter stations with constant current control. **07**

- Q.4** (a) Give analysis of 12 pulse converter with proper diagrams. **07**
- (b) In view of reactive power control, explain working of synchronous condensers with schematic diagram. **07**

OR

- Q.4** (a) Explain different methods of reactive power control. **07**
- (b) Discuss advantages of FACTS. **07**

- Q.5** (a) Explain the necessity of VDCOL control used in HVDC systems with proper characteristics diagrams. **07**
- (b) Give brief comparison of different SVCS. **07**

OR

- Q.5** (a) Explain Thyristor Controlled Transformer (TCT) compensator. **07**
- (b) Draw schematic diagram of HVDC transmission system and explain working of each component in brief. **07**
