

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III • EXAMINATION – SUMMER 2013****Subject Code: 131101****Date: 31-05-2013****Subject Name: Basic Electronics****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Q.1 (a) Define electron volt and draw general energy band diagram for insulator, semiconductor, and metal. **07**

(b) State Bohr's postulates and derive expression for energy levels of electrons in Joules as a function of orbit number surrounding nucleus. **07**

Q.2 (a) Explain the term mobility related to charged carriers and derive expression for point form of Ohm's law. **07**

(b) Describe phenomenon of Hall effect with mathematical derivations. What are the different applications of Hall effect? **07**

OR

(b) Obtain expression for potential difference across a semiconductor with non-uniform (graded) doping. Using the same, derive an expression for potential difference across open-circuited step-graded p-n junction. **07**

Q.3 (a) Define and explain following terms related to diode: 1. Transition capacitance and 2. Diffusion capacitance. **07**

(b) Draw double-diode clipper circuit which limits output voltage at two independent levels. Explain its working with necessary waveforms. **07**

OR

Q.3 (a) Draw diode I-V characteristic and explain diode static and dynamic resistances. **07**

(b) Explain working full-wave rectifier with necessary waveforms. Obtain expression for dc output voltage. **07**

Q.4 (a) Indicate and briefly explain various current components flowing in p-n-p transistor with forward-biased emitter junction and reverse-biased collector junction. **07**

(b) Define h-parameters, and draw h-parameter equivalent circuit for CE, CB and CC configured transistor. **07**

OR

Q.4 (a) Draw output and input characteristics for common-base configured transistor. Explain base-width modulation (Early effect) for the same. **07**

(b) Derive expression for small-signal voltage gain of emitter follower circuit in terms of h-parameters. **07**

Q.5 (a) What do you understand by bias stability in transistor amplifier circuit? Explain thermal instability of bias point for the same. **07**

(b) Draw structure of n-channel JFET and explain its working. **07**

OR

Q.5 (a) Draw and explain working of diode compensation circuit for V_{BE} for self-stabilization in amplifier circuit. **07**

(b) Compare FET and BJT devices. Define small-signal parameters of FET and draw low-frequency small-signal model for the same. **07**
