

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-V • EXAMINATION – SUMMER 2013****Subject Code: 151003****Date: 16-05-2013****Subject Name: Integrated Circuits and Applications****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) 1. Draw block diagram of a typical op-amp and explain functions of each block. **04**  
2. Define followings for an op-amp: (i) input offset current (ii) CMRR (iii) Differential input resistance. **03**  
(b) What type of feedback is present in the non-inverting amplifier? Derive expression for voltage gain, input resistance, output resistance and bandwidth of a non-inverting amplifier using a non ideal op-amp. **07**

- Q.2** (a) 1. Draw inverting amplifier. Determine the maximum output offset voltage due to (i) input offset voltage  $V_{io}$  and (ii) input bias current  $I_B$ . Take  $V_{io\ max} = 6\ mV\ dc$ ,  $I_B\ max = 500\ \mu A\ dc$ ,  $V_s = \pm 15\ V$ ,  $R_F = 47\ k\Omega$  and  $R_1 = 470\ \Omega$ . **04**  
2. What is slew rate? List causes of slew rate. Also explain its significance in applications. **03**  
(b) Draw peaking amplifier specify the value of all components to provide a gain of 10 at a peak frequency of 16 KHz. Take  $L = 10\ mH$  with internal resistance of  $30\ \Omega$ . **07**

**OR**

- (b) What is an instrumentation amplifier? Explain with the help of neat diagram the operation of an instrumentation amplifier employing three basic op-amps and with provision for variation in the voltage gain. **07**

- Q.3** (a) Draw the non-inverting Schmitt trigger comparator circuit and explain the threshold levels and hysteresis. **07**  
(b) Draw asymmetrical square-wave generator circuit using op-amp. Specify suitable component value for the following specification:  $T_{ON} = 1\ sec$ .  $T_{OFF} = 2\ sec$ . Assume value of  $\beta = 0.1$  and  $C = 100\ \mu F$ . **07**

**OR**

- Q.3** (a) Explain in detail operation of full-wave precision rectifier with neat diagram and waveform. **07**  
(b) Draw basic log amplifier using a transistor. Derive the expression for output voltage. Also state disadvantages of circuit. **07**

- Q.4** (a) Design second order Butterworth low pass filter with  $\approx 3\ dB$  frequency of 10 KHz. Choose  $C = 1\ \mu F$ . ( Use equal component KRC filter circuit) **07**  
(b) With the help of a circuit diagram explain the operation of first order high-pass filter. **07**

**OR**

- Q.4 (a)** Design a wide-band band pass filter using a single op-amp for  $f_L = 100$  Hz,  $f_H = 1$  KHz and pass band gain of 4. Also calculate the value its quality factor Q. **07**
- Q.4 (b)** Derive the expression for filter transfer function of a first order low-pass filter and draw its frequency response characteristics. **07**
- Q.5 (a)** Design a free running ramp generator using IC 555 for  $V_{CC}=10$  V,  $C=0.1\mu\text{F}$  and period  $T= 2$  ms. Take transistor with  $\beta = 100$ . Explain its working. **07**
- (b)** Draw block diagram of the PLL system and explain function of each block. State the applications of PLL. **07**
- OR**
- Q.5 (a)** Draw circuit diagram of an astable multivibrator using IC 555 and explain its operation. Derive expression for frequency of operation and duty cycle. **07**
- (b)** Draw block diagram of a basic SMPS and explain it. Also state advantages and disadvantages of SMPS. **07**

\*\*\*\*\*