

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V • EXAMINATION – SUMMER 2013****Subject Code: 151703****Date: 20-05-2013****Subject Name: Electronics in Industries****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain fast recovery diode with its transient response. Describe schottky diode with its characteristic. **07**
- (b) What are the different methods to turn on the SCR? Explain each in detail. **07**

- Q.2** (a) Describe three-phase double-star rectifier with waveforms. **07**
- (b) Explain six phase half wave uncontrolled rectifier with waveforms. Find ripple factor of the circuit. **07**

OR

- (b) Explain three-phase fully-controlled bridge controlled rectifier with help of waveforms. Derive its average output voltage equation. **07**

- Q.3** (a) Give the difference between power MOSFET and power BJT. Classify the power MOSFET. Explain depletion type MOSFET with output and transfer characteristics. **07**
- (b) Explain dynamic and static characteristics of IGBT with its construction. **07**

OR

- Q.3** (a) Explain dynamic turn-on and off characteristics of SCR. **07**
- (b) What are the difference between SCR and TRIAC? Explain TRIAC construction and working in details. **07**

- Q.4** (a) Give the difference between UJT and PUT. Explain UJT synchronized firing circuit for SCR. **07**
- (b) What is the commutation circuit? Explain voltage and current commutation circuit in detail. **07**

OR

- Q.4** (a) Explain gate characteristic of SCR. **07**
- Q.4** (b) Explain the protection circuit of power semiconductor devices for overvoltage and gate. **07**

- Q.5** (a) Draw and explain the waveforms of half-wave controlled rectifier with inductive load and flywheel diode. Derive the average dc output for it. **07**
- (b) A 60V, 50 Hz AC supply with 1:3 transformer ratio applied to the single phase bridge uncontrolled rectifier having resistive load of $1K\Omega$. Calculate the dc output voltage, dc current, rms output voltage, ripple factor, PIV rating of the diode and dc output power. **07**

OR

- Q.5** (a) What are the advantages and disadvantages of dual converter? Explain dual converter in detail with waveforms. **07**
- (b) A three phase half-wave controlled rectifier is connected to a 220 V, 50 Hz as supply with a 200Ω load resistance. If the firing angle $\alpha = 60^\circ$ calculate the average output voltage, current and power. **07**
