

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII • EXAMINATION – SUMMER 2013****Subject Code: 172403****Date: 28-05-2013****Subject Name: Power Processing Circuits - II****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain single-phase full-bridge inverter circuit with resistive load. Draw output waveforms if load is R-L, R-L-C over damped and R-L-C under damped. **07**
- (b) Explain active front-end rectifier with block diagram. List disadvantages of controlled rectifier and advantages of active front-end rectifier. **07**
- Q.2** (a) Explain five-level diode-clamped single-phase multilevel inverter with circuit diagram and waveforms. **07**
- (b) Explain single-phase capacitor commutated CSI having resistive load with circuit diagram and waveforms. **07**
- OR**
- (b) Explain the single-phase parallel inverter with circuit diagram and waveforms. **07**
- Q.3** (a) Explain the three-phase 180° mode VSI with circuit diagram and waveforms. **07**
- (b) Explain single-phase ac voltage controller having R-L load with circuit diagram and waveforms. Derive expression for the load current i_o . **07**
- OR**
- Q.3** (a) Explain ZVS resonant converter with circuit diagram and waveforms. **07**
- (b) Explain the single-phase to single-phase step-down midpoint cycloconverter considering continuous load current with circuit diagram and waveforms. **07**
- Q.4** (a) Explain external control of dc input voltage and ac output voltage methods for the control of output voltage of inverter. **07**
- (b) Explain phase dead banding and triplen injection modulation. Draw necessary waveforms. **07**
- OR**
- Q.4** (a) Explain multiple-pulse width modulation technique used for voltage control of single-phase inverters. **07**
- (b) Explain switching states and space vector diagram for two-level inverter. **07**
- Q.5** (a) Explain integral cycle control method used for voltage control in ac voltage controllers. Derive equation for rms value of output voltage and thyristor current. **07**
- (b) Draw the block diagram of a typical battery charger and explain each block in brief. Explain trickle charging. **07**
- OR**
- Q.5** (a) Explain the modified Mc-Murray half-bridge inverter with circuit diagram and waveforms. **07**
- (b) Define UPS. Draw the detailed block diagram of UPS. Give the comparison of off-line and on-line UPS. **07**
