

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III • EXAMINATION – SUMMER • 2014****Subject Code: 131101****Date: 30-05-2014****Subject Name: Basic Electronics****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Explain Hall effect phenomenon and list out its applications. Quantitatively discuss the use of Hall effect to determine mobility. **07**
- (b)** Derive continuity equation for carrier concentration in body of a semiconductor. **07**
- Q.2 (a)** Discuss the process of splitting of energy levels of isolated atoms into energy bands as these atoms are brought into close proximity to form a crystal. **07**
- (b)** Draw diode I-V characteristic, discuss its temperature dependence and obtain expression for diode dynamic resistance. **07**
- OR**
- (b)** Explain working of Tunnel diode. Draw its I-V characteristic and symbol. List out applications of Tunnel diode. **07**
- Q.3 (a)** For a sinusoidal input of 10 V peak, sketch I_R and V_O in the circuit shown in Fig. Q. 3 (a). Assume ideal diode with cut-in voltage equal to 0.7 V. **07**
- (b)** Draw BJT circuit in common-base configuration as well as its input and output characteristics. Explain base-width modulation for the same. **07**
- OR**
- Q.3 (a)** A symmetrical 5 KHz square wave that varies between + 10 V and -10 V is impressed upon the clipping circuit shown in Fig. Q: 3(a) OR. Assume for diode: R_f (forward bias resistance) = 0, R_r (reverse bias resistance) = 2 M Ω , Cut-in voltage = 0. Sketch the steady state output waveform, indicating value of maximum, minimum, and constant portion. **07**
- (b)** In diode connected transistor circuit shown in Fig. Q: 3 (b) OR, the transistor has $\beta = 19$. If $V_E = 4$ V, determine the value of R_B . Neglect base-to-emitter junction voltage in the calculations. **07**
- Q.4 (a)** Derive expression for A_i , A_v , Z_i , and Y_o for a basic amplifier circuit in terms of h-parameters. **07**
- (b)** What do you understand bias compensation? Draw and explain diode compensation circuit for V_{BE} . **07**
- OR**
- Q.4 (a)** Derive expression for A_i , A_v , Z_i , and Y_o for a common-collector amplifier circuit using simplified hybrid model. **07**
- (b)** Explain thermal runaway. Show graphically that thermal runaway cannot take place if the quiescent point is located at $V_{CE} < (1/2) V_{CC}$. **07**
- Q.5 (a)** Draw two-dimensional structure of n-channel MOSFET. Explain its working. **07**
- (b)** Explain push-pull arrangement of transistors and discuss its advantages. **07**
- OR**
- Q.5 (a)** Explain the use of FET as a voltage variable resistor. **07**
- (b)** Draw transformer-coupled audio amplifier circuit. Show that the maximum value of conversion efficiency for this circuit is 50 %. **07**

