

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V • EXAMINATION – SUMMER • 2014****Subject Code: 151003****Date: 13-06-2014****Subject Name: Integrated Circuits and Applications****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Parameters of 741 IC are: A (open loop gain) = 2×10^5 , $R_i = 2 \text{ M}\Omega$, $R_o = 75 \Omega$, $f_o \approx 5 \text{ Hz}$, Supply voltages = $\pm 15 \text{ V}$, output voltage swing = $\pm 13 \text{ V}$.

- Q.1** (a) (1) Op-amp (741) IC with an open loop gain equal to 2×10^5 is used in open loop mode. Supply voltage is $\pm 15 \text{ V}$. Find out output voltage if (a) $V_{id} = -20 \text{ mV}$, and (b) $V_{id} = 50 \mu\text{V}$. V_{id} is input differential voltage across positive and negative input terminals of op-amp. **07**
- (2) Define following terms for op-amp: (a) CMRR, (b) SVRR, (c) Slew Rate, and (d) Output voltage swing.
- (b) Design non-inverting op-amp (741) based amplifier which has feedback resistance (R_F) equal to $10 \text{ k}\Omega$ and closed loop gain of 11. For this circuit, calculate R_{iF} , R_{oF} , f_F , and V_{ooT} (total output offset voltage with feedback). **07**
- Q.2** (a) Draw two op-amp based differential amplifier and derive expression for its gain, input and output resistances, and bandwidth. **07**
- (b) Discuss design steps for input offset voltage compensating network. **07**
- OR**
- (b) For an inverting amplifier with a gain equal to -100 and feedback resistance of $47 \text{ k}\Omega$, determine maximum possible output offset voltage due to (1) input offset voltage of 6 mV , and (2) Input bias current of 500 nA . What value of R_{OM} is needed to reduce offset voltage effect due to the effect of input bias current? **07**
- Q.3** (a) Draw schematic of single supply based op-amp AC inverting amplifier. Explain its working along with necessary input and output waveforms. **07**
- (b) Design a practical op-amp based integrator such that peak gain is 20 dB and the gain is 3 dB down from its peak value at ω equal to $10,000 \text{ rad/s}$. Use capacitance of $0.01 \mu\text{F}$. **07**
- OR**
- Q.3** (a) Describe the operation of differential instrumentation amplifier which uses resistive transducer in a bridge circuit. Show that the output voltage is directly proportional to the change in resistance value of a transducer. **07**
- (b) Draw and explain working of basic differentiator circuit. What are the limitations of this circuit? How it can be corrected? **07**
- Q.4** (a) Explain working of op-amp based Schmitt trigger circuit along with schematic and input/output waveforms. **07**
- (b) Illustrate operation of op-amp based triangular wave generator circuit with necessary waveforms as well as mathematical steps. **07**
- OR**
- Q.4** (a) Draw op-amp based full wave rectifier (absolute-value) circuit. Explain its working with necessary input/output waveforms. **07**
- (b) Discuss operation of op-amp based saw-tooth wave generator circuit with relevant diagram and waveforms. **07**

- Q.5** **(a)** Describe operation of each block of phase locked loop. List out PLL applications. **07**
- (b)** Draw Sallen-key low-pass filter circuit and obtain its transfer function. **07**
- OR**
- Q.5** **(a)** Draw 555 timer block diagram. Explain its working and its use as a monostable multivibrator. **07**
- (b)** Sketch Delyiannis-Friend circuit and obtain its transfer function. **07**
