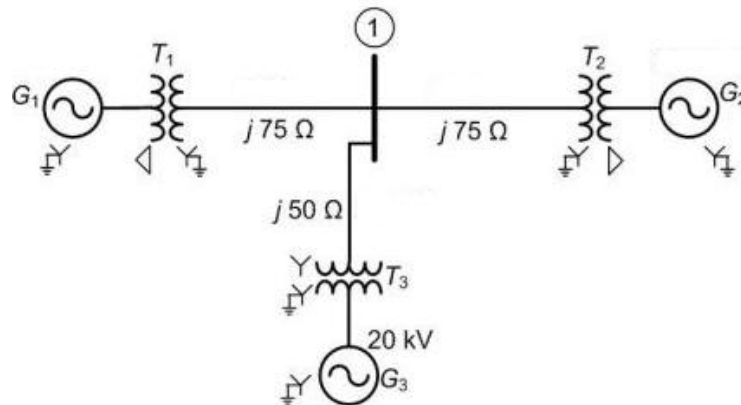


GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII • EXAMINATION – SUMMER • 2014****Subject Code: 170807****Date: 31-05-2014****Subject Name: Power System Analysis****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Give the merits and demerits of per unit system. Prove that the per-unit impedance of a transformer is the same regardless of the side from which it is viewed. **07**
- (b)** Consider the 50 Hz power system the single-line diagram of which is shown in Figure. The system ratings are: **07**
- Generator G_1 : 200 MVA, 20 kV, $X_d = 15\%$
 Generator G_2 : 300 MVA, 18 kV, $X_d = 20\%$
 Generator G_3 : 300 MVA, 20 kV, $X_d = 20\%$
 Transformer T_1 : 300 MVA, 220Y/22 kV, $X = 10\%$
 Transformer T_2 : Three single-phase units each rated 100 MVA, 130Y/25 kV, $X = 10\%$
 Transformer T_3 : 300 MVA, 220/22 kV, $X = 10\%$
 The transmission line reactances are as indicated in the figure. Draw the reactance diagram choosing the Generator 3 circuit as the base.




- Q.2 (a)** With the simplifying assumptions explain the SC transient on a transmission line and hence prove that; $I_{mm} \text{ (max. possible)} = 2[\sqrt{2}V/|z|]$, i.e. doubling effect. Also draw necessary waveforms to explain doubling effect. **07**
- (b)** Explain different types of current limiting reactors. Show how they are connected at power stations. Write their uses also. **07**
- OR**
- (b)** Explain how an unbalanced set of three phase voltages can be represented by systems of balanced voltages. **07**

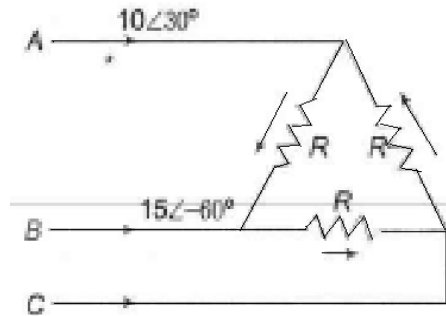- Q.3 (a)** Two synchronous motor are connected to the bus of a large system through a short transmission line as shown in figure. the rating of components are : **07**
 Motors (each): 1 MVA, 440 V, 0.1 p.u. transient reactance.
 Line: 0.05 ohm reactance.
 Large system: short circuit MVA at its bus at 440 V is 8.
 when the motors are operating at 440 V, calculate the short circuit symmetrical current fed into a 3-phase fault at motor bus.



- (b)** A delta connected balanced resistive load is connected across an unbalanced three phase supply as shown in figure. With currents line A and B specified. Find the symmetrical components of line currents. **07**



OR


- Q.3 (a)** What are the causes of unsymmetrical faults in power system? Derive an expression for the fault current for a single line-to-ground fault. **07**
(b) Justify the following statement: **07**
 “For a fault at alternator terminals, a single line to ground fault is generally more severe than a 3-ph fault whereas for faults on transmission lines, a 3-ph fault is more severe than other faults.”

- Q.4 (a)** Derive the power angle equation: $P = (E_G E_M / X) \sin \delta$ with usual notations. Also draw the power angle curve. **07**
(b) A synchronous generator of reactance 1.20 p.u. is connected to an infinite bus ($|V| = 1$ p.u.) through transformers and a line of total reactance of 0.60 p.u. The generator no load voltage is 1.20 p.u. and its inertia constant is $H = 4$ MW-s/MVA. The resistance and machine damping may be assumed negligible. The system frequency is 50 Hz. Calculate the frequency of natural oscillations if the generator is loaded to (i) 50% and (ii) 80% of its maximum power limit. **07**

OR

- Q.4 (a)** Derive the equation $Y_{bus} = A^t Y A$, Where Y_{bus} = bus admittance matrix, A = bus incidence matrix, A^t = transpose of A and Y = primitive admittance matrix. **07**

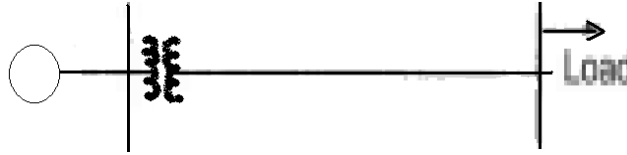- (b) For the system of figure. Find the voltage at the receiving bus at the end of the first iteration. Load is $2 + j0.8$ p.u. Voltage at the sending end (slack) is $1 + j0$ p.u. Line admittance is $1.0 - j4.0$ p.u. Transformer reactance is $j0.4$ p.u. Off-nominal turns ratio is $1/1.04$. Use the GS technique. Assume $V_R = 1 \angle 0^\circ$. 07



- Q.5 (a) Discuss the advantages and limitations of Gauss-Seidal and Newton Raphson methods. Of this two, which method is generally preferred for solving the load flow problem? 07

- (b) What are the conditions to be satisfied before a 3-phase alternator is synchronized to infinite bus bars? 07

OR

- Q.5 (a) Explain how the active and reactive power loading of an alternator working on infinite bus-bar is controlled. 07

- (b) Describe briefly the principle of operation of load dispatch organization coordinating different types of power plants in a power system. 07
