

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII • EXAMINATION – SUMMER • 2014****Subject Code: 172401****Date: 22-05-2014****Subject Name: Power Electronics Systems Modeling****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw and Explain the block diagram of Power Electronics System with reference to modeling. **07**
 (b) State inductor volt-second balance principle and explain its use in buck converter. **07**
- Q.2** (a) Explain DC transformer model with necessary equations and figures. **06**
 (b) Find out the steady state output voltage for a buck chopper using small-ripple approximation. Draw necessary diagrams & waveforms. Also derive the equation for voltage conversion ratio $M(D)$ and draw its graph. **08**
- OR**
- (b) For a given buck converter, if the input voltage is 50 V, Mark Space Ratio is 0.25, Switching frequency is 100 kHz and load resistance is $10\ \Omega$, calculate the value of V_o and I . Also find out the value of C such that the peak output voltage ripple ΔV is 5% of V_o . **08**
- Q.3** (a) Discuss different types of modeling methods with their merit and demerits. **07**
 (b) List the major steps of engineering design process. Explain each in brief. **07**
- OR**
- Q.3** (a) What do you mean by small signal approximation? Explain with appropriate example. **06**
 (b) Why is AC modeling required? Discuss non-linearity in electrical system. Explain perturbation and linearization w.r.t. power electronics. **08**
- Q.4** (a) Develop the state space model of a buck converter. Draw necessary figures. **08**
 (b) Define the following: Modeling, Controllability, SISO, Normalization, Impulse Response, Linearization **06**
- OR**
- Q.4** (a) Explain the difference between ideal and physical models of AC transformer. Draw neat diagrams. **06**
 (b) Develop the state space model of a boost converter along with necessary figures. **08**
- Q.5** (a) What is Canonical Circuit Model? Explain the manipulation of buck-boost converter model into canonical form. **07**
 (b) Explain the graphical construction of series impedances using a series R-C network. **07**
- OR**
- Q.5** (a) Explain the close loop speed control of DC motor using power electronics converter. **07**
 (b) Explain the state space model of a full bridge inverter. **07**
