

GUJARAT TECHNOLOGICAL UNIVERSITY**B. E. Sem. - V - Examination – June- 2011****Subject code: 152403****Subject Name: Applied Power Electronics****Date: 24/06/2011****Time: 10:30 am – 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain LOG amplifier circuit as analog processing circuit. **07**
 (b) Write brief note on Power Electronics and its requirements. **07**
 Also enlist its applications.

- Q.2** (a) What is cause of low power factor? Explain power factor correction with appropriate circuit. **07**
 (b) Write technical note on static VAR compensation. **07**

OR

- (b) Explain off-line UPS with block diagram. **07**

- Q.3** (a) Describe High pass filter circuit. **07**
 (b) Explain biquad filter in brief. **07**

OR

- Q.3** (a) Explain controlled rectifier as a basic power modulator. **07**
 (b) Explain any one charging method for battery. State its advantages and disadvantages. **07**

- Q.4** (a) Explain induction heating as an industrial application. **07**
 (b) Discuss Electroplating process. **07**

OR

- Q.4** (a) Write technical note on LED lighting. **07**
 (b) Describe fan regulator circuit. **07**


- Q.5** (a) Explain basic principle of DC drive. **07**
 (b) Solve following through analog circuit. **07**

$$x+y=10$$

$$2x+3y=5$$

OR

- Q.5** (a) Explain basic concept of switched capacitor circuit. Also draw inverting amplifier circuit based on it. **07**
 (b) In Fig.1 switch k is turned on and off with frequency f. Explain how does fixed DC to variable DC conversion take place? **07**

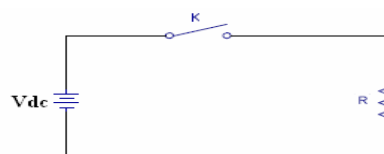**Fig.1**
