

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III • EXAMINATION – WINTER • 2014****Subject Code: 2132003****Date: 20-12-2014****Subject Name: Design Concepts in Basic Electronics****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.


- Q.1 (a)** Answer the following question. **07**
- (1) Define Digital Signal.
 - (2) Convert $(145)_{10}$ into its equivalent Binary.
 - (3) Convert $(10010101110)_2$ into its equivalent Octal and Hexadecimal number.
 - (4) Convert $(1F67.546)_{16}$ into its equivalent Decimal.
 - (5) Convert $(6)_{10}$ into its equivalent BCD, Gray code and Excess-3 code.
 - (6) State the truth table of Full-Adder.
 - (7) State excitation table and characteristics table for J K Flip Flop.
- (b)** Prove the following using Truth Table. **07**
- (1) $\bar{A} + \bar{B} + \bar{C} = \overline{(A \cdot B \cdot C)}$
 - (2) $XY + \bar{X}Z + YZ = XY + \bar{X}Z$
- Q.2 (a)** Explain in detail different type of breakdown in diode. **07**
- (b)** Simplify the following Boolean function using Karnaugh map method and realize with minimum NAND gates only. **07**
- Function $F(A,B,C,D) = \sum (0,1,2,8,9)$ and don't care conditions: $d(A,B,C,D) = \sum (3, 5,10,13)$

OR


- (b)** Reduce following Boolean expression in minimum number of literals. **(ANY TWO)** **07**
- (1) $AB + A(B + C) + B(B + C)$
 - (2) $\bar{X}YZ + XZ + \bar{X}Z$
- Q.3 (a)** Design 3 bit up – down synchronous counter with help of T flip flop. **07**
- (b)** Give the points of difference between half wave, Full wave, and Bridge rectifier. **07**

OR

 - Q.3 (a)** Show that NAND and NOR are universal gate. **07**
- (b)** The diodes are ideal, plot V_o against V_i indicating all intercepts, slopes and voltage levels for Fig. and Sketch V_o if $V_i = 40 \sin \omega t$. **07**



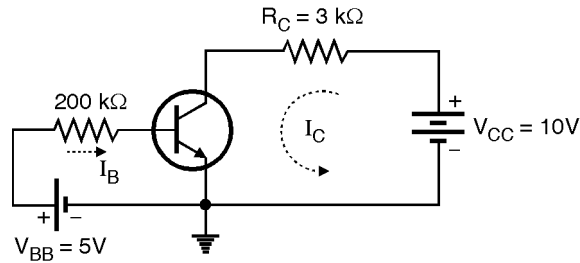- Q.4 (a)** Explain with neat diagram working of 8x1 multiplexer and 3to8 decoder. **07**
- (b)** For the transistor shown in Fig, $\beta = 100$. Find the transistor currents and state in which region it is operating. Assume that it is a silicon transistor **07**



OR

- Q.4 (a)** Explain with neat diagram working of 4-bit bidirectional shift register with parallel load **07**
- (b)** Explain in details effect of temperature, transistor and collector current on β_{dc} **07**
- Q.5 (a)** Explain the input output characteristic of n-p-n transistor in CE configuration. Also indicate different regions. **07**
- (b)** Explain with neat diagram Voltage divider bias **07**

OR

- Q.5 (a)** Explain the input output characteristic of n-p-n transistor in CB configuration. Also indicate different regions. **07**
- (b)** The fixed bias circuit of Fig. a silicon transistor is uses. The component values are $R_C = 500 \Omega$ and $R_B = 100 \text{ k}\Omega$. β_{dc} of the transistor is 100 at 30°C . Determine Q point co-ordinates at 30°C . **07**

