

GUJARAT TECHNOLOGICAL UNIVERSITY
B. E. - SEMESTER – IV • EXAMINATION – WINTER 2012

Subject code: 141101**Date: 28/12/2012****Subject Name: Advance Electronics****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** State the behavior of transistor at high frequencies and explain why we cannot use the h-parameters for the analysis at high frequencies. **07**
- (b)** Explain the classification of amplifiers based on position of operating point(Q – point). **07**
- Q.2 (a)** State the advantages, disadvantages and applications of RC coupled amplifiers. **07**
- (b)** Explain the advantages and disadvantages of negative feedback. **07**
- OR**
- (b)** Define the following terms: : **07**
(1) Slew rate (2) CMRR (3) PSRR (4) Noise margin (5) fan-in
(6) Gain bandwidth product (7) Figure of merit for logic families
- Q.3 (a)** Give the complete Classification of Oscillators. **07**
- (b)** Design RC phase shift oscillator for the frequency of 6 kHz. **07**
- OR**
- Q.3 (a)** State and explain any seven characteristics of an ideal Op-Amp. **07**
- (b)** Draw and explain the block diagram of an Op-Amp. **07**
- Q.4 (a)** State the advantages and disadvantages of TTL. **07**
- (b)** Draw the symbol and AC equivalent circuit of a Crystal oscillator and explain the principle of operation of Crystal Oscillator. **07**
- OR**
- Q.4 (a)** Using an OP-AMP, draw the functional diagram of a successive approximation ADC and explain its working. **07**
- (b)** What is Digital to Analog Converter? Draw and Explain R-2R DAC. **07**
- Q.5 (a)** Classify the logic families. Give comparisons with the advantages and disadvantages of each logic families. **07**
- (b)** A quartz crystal has following constants: $L = 0.06 \text{ H}$, $C_1 = 0.01 \text{ pf}$, $C_2 = 12 \text{ pf}$ and $R = 500 \Omega$. Calculate the values of series and parallel resonant frequencies. (Here C_1 is the capacitor in the equivalent circuit of crystal and C_2 is the mounting capacitance.) **07**
- OR**
- Q.5 (a)** Explain Dual slope A/D converter. **07**
- (b)** Switched capacitor type DAC. **07**
