

GUJARAT TECHNOLOGICAL UNIVERSITY**B.E. - SEMESTER – VIII EXAMINATION – OCTOBER 2012****Subject code: 180304****Date: 25/10/2012****Subject Name: Electronic System Design****Time: 02.30pm - 05.00pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain the two transistor analogy of SCR. **07**
(b) State the definition and importance of EMC. Explain different E field and H field coupling briefly. **07**
- Q.2** (a) Describe the forward characteristics of SCR. **07**
(b) Explain the working principle of PM step motor. **07**
- OR**
- (b) Explain the working principle of VR step motor. **07**
- Q.3** (a) Explain the step down chopper in detail. Derive the equation for its duty cycle. **07**
(b) Write a short note of PWM inverter. **07**
- OR**
- Q.3** (a) What is step up chopper? Draw and explain the flux, current and voltage waveform for it. **07**
(b) Write a short note on series resonance inverter. **07**
- Q.4** (a) Explain any two commutation methods for SCR **07**
(b) Write a short note on Power MOSFET. **07**
- OR**
- Q.4** (a) Explain different turn on methods for SCR. **07**
(b) Write a short note on IGBT. **07**
- Q.5** (a) Write short note on effect of shield on electric field coupling. **07**
(b) What is SMPS? Draw & explain its block diagram. **07**
- OR**
- Q.5** (a) Explain different grounding methods briefly. **07**
(b) Write a short note on UPS. **07**
