

GUJARAT TECHNOLOGICAL UNIVERSITY
BE SEMESTER - V - EXAMINATION – WINTER 2013

Subject Code: 151006**Date: 09/12/2013****Subject Name: Applied Electronics****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Define the following terms: CMRR, Slew rate, Transducer, Photoemission effect, Intrinsic standoff ratio(η), Duty cycle, Multiplexer **07**
(b) Draw and Explain the working of SMPS with required block diagram circuits and wave forms. Enlist differences between linear and switch mode regulator. **07**
- Q.2** (a) What are the advantages of close loop configuration? Derive expression of close loop gain for Non-inverting configuration of Op-Amp. **07**
(b) An op-Amp is used in inverting mode with $R_1=2K\Omega$, $R_F=30K\Omega$, $V_{cc}=\pm 15V$. Calculate the output voltage for the given inputs: 1) $V_{in}=100mV$ 2) $V_{in}=3V$. **07**
- OR**
- (b) Draw and explain Block diagram and voltage transfer characteristics of an Ideal Op-amp. What is virtual ground concept? **07**
- Q.3** (a) Describe the steps to convert an Astable multivibrator in a square wave oscillator using a diode. **07**
(b) State different types of temperature transducers. Explain them in brief. **07**
- OR**
- Q.3** (a) Derive the expression of pulse width for monostable multivibrator. Design a monostable multivibrator using IC 555 for $V_{cc}=12V$ and pulse width of 1msec. **07**
(b) Write a short note on piezoelectric transducer. **07**
- Q.4** (a) What is Liquid Crystal Display? State and explain different types of LCD. **07**
(b) Compare SCR with triac. Explain SCR with all necessary diagrams. **07**
- OR**
- Q.4** (a) Explain the optocoupler/Isolator in details. Also explain one application. **07**
(b) Explain the working of DIAC(Diode A.C. Switch) with equivalent circuit and I-V characteristics of it. **07**
- Q.5** (a) Explain the principle of Digital Storage Oscilloscope with block diagram. **07**
(b) What is fuzzy logic? Explain CD technology with block diagram. **07**
- OR**
- Q.5** (a) What is sequential circuit? Compare sequential circuit with combinational circuit. Explain A/D converter. **07**
(b) Explain the 8051 architecture in detail **07**
