

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII • EXAMINATION – WINTER • 2014****Subject Code: 172401****Date: 25-11-2014****Subject Name: Power Electronics Systems Modeling****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Discuss the concept of nonlinearity and the importance of perturbation & linearization with respect to power electronics giving an example. **07**
- (b)** Discuss different types of modeling methods with their merit and demerits. **07**
- Q.2 (a)** Derive the expression of duty cycle for boost converter with the help of capacitor charge second principle. **07**
- (b)** Develop the model of Armature controlled DC servo motor. **07**
- OR**
- (b)** Explain DC transformer model with necessary equations and figures. **07**
- Q.3 (a)** Explain the modeling the boost converter inclusion inductor copper loss. Draw the waveform for inductor voltage and capacitor current waveforms. **07**
- (b)** Derive small signal linearized equation that describes change in inductor current. **07**
- OR**
- Q.3 (a)** Explain the modeling of boost converter inclusion of semiconductor conduction losses. Draw the waveform for inductor voltage and capacitor current. **07**
- (b)** Show that during transient period net change in inductor current over one switching period can be correctly predicted by use of average inductor voltage. **07**
- Q.4 (a)** Find out the steady state output voltage for a boost chopper using small-ripple approximation. Draw necessary diagrams & waveforms. Also derive the equation for voltage conversion ratio $M(D)$ and draw its graph. **07**
- (b)** What is a Transfer Matrix & how it is obtained from state-space equations? **07**
- OR**
- Q.4 (a)** Find out the steady state output voltage for a buck chopper using small-ripple approximation. Draw necessary diagrams & waveforms. Also derive the equation for voltage conversion ratio $M(D)$ and draw its graph. **07**
- (b)** How the review of bode plot is useful in analysis of converters? **07**
- Q.5 (a)** What is feedback control? Explain the closed loop of controlled rectifier with necessary circuit diagram and waveform. **07**
- (b)** Find the state-space model of the second-order differential equation. **07**
- $$\ddot{x} + a\dot{x} + bx = f(t).$$
- OR**
- Q.5 (a)** What is linearization? Explain linearized circuit for an up/down converter in discontinuous conduction using necessary circuit, equation and waveform. **07**

(b) Derive state space for the following circuit diagram.

