

GUJARAT TECHNOLOGICAL UNIVERSITY**B.E. Sem-IV Examination June- 2010****Subject code: 142402****Subject Name: Fundamental of Power Electronics****Date: 21 /06 /2010****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.


- Q.1** (a) Explain the operation of center-tap controlled rectifier and draw its input and output waveforms. **07**
- (b) What is Power Electronics? Discuss briefly the concept of Power Electronics System with block diagram. **07**
- Q.2** (a) In a full wave rectifier, the load resistance is $5K\Omega$. The input voltage to each diode is $200\sin 2\pi 50t$. Calculate the maximum value of current, the Average current, the rms current, DC power output, Form factor and Ripple factor. **07**
- (b) What is Power diode? Discuss V-I characteristics of Power diode and Ideal diode. **07**

OR

- (b) Describe the switching characteristics of Power MOSFET. **07**
- Q.3** (a) With the help of block diagram explain the working of Switch Mode Power Supply. **07**
- (b) Explain the Four mode operation of TRIAC with the help of its V-I characteristics. **07**

OR

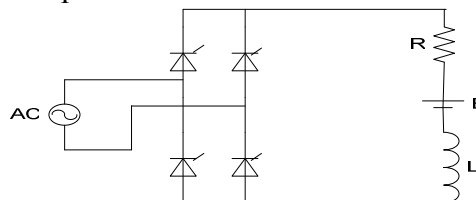- Q.3** (a) As shown in figure, 1-phase full converter is supplied by a 230V, 50Hz input. If $\alpha = \pi/3$, $E = 10V$, $R = 10\Omega$, $L = 20mH$. Determine the Average output voltage, output current and load impedance. **07**



- (b) Explain construction and working of thyristor using two transistor analogy. **07**
- Q.4** (a) Explain the operation of Uni-Junction Transistor (UJT) with basic application circuits. **07**
- (b) With necessary waveforms describe the working of 1-phase full bridge inverter for RLC under damped and over damped load. **07**

OR

- Q.4** (a) Discuss merits and demerits of Thyristor based chopper. **07**
- (b) Explain the working of McMurray-Bedford Half bridge inverter with waveforms. **07**
- Q.5** (a) State the principle of 1-phase to 1-phase step-up cyclo-converter with the help of mid point and bridge type configurations. **07**
- (b) State the control strategies for the regulation of output voltage in a. c. voltage controller. **07**

OR

- Q.5** (a) Explain the operation of single phase semi converter assuming continuous current & draw various waveforms for $\alpha = 45^\circ$. **07**
- (b) Write a comprehensive note on protections of Thyristor. **07**
