

GUJARAT TECHNOLOGICAL UNIVERSITY**B. E. Sem. - V - Examination – June- 2011****Subject code: 151006****Subject Name: Applied Electronics****Date: 30/06/2011****Time: 10:30 am – 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw the block diagram of a regulated d.c. power supply and explain briefly the function of each block. **07**
 (b) Draw the block diagram of an OP-AMP and explain the function of each block. **07**
- Q.2** (a) Explain the operation of an astable multivibrator using IC 555. Draw its circuit diagram and waveforms. **07**
 (b) Define the following parameters. **07**
 1) Common Mode Rejection Ratio (CMRR)
 2) Latching current (I_L) of an SCR.
 3) Trace period and retrace period of C.R.T.
- OR**
- (b) With the help of the block diagram, explain the operation of a single trace Cathod Ray Oscilloscope. (CRO) **07**
- Q.3** (a) Derive the expression of OP-AMP for non-inverting closed loop voltage gain. (A_{vf}) **07**
 (b) Explain the construction and operating principle of a semiconductor strain gauge. State its advantages and applications. **07**
- OR**
- Q.3** (a) Define intrinsic stand off ratio (η) of UJT and explain its use as relaxation oscillator. Draw the relevant waveforms. **07**
 (b) Explain construction and principle of operation of photoconductive cell. **07**
- Q.4** (a) Explain in detail the half adder and full adder circuit using logic diagram. **07**
 (b) Design a monostable 555 timer circuit to produce an output pulse 165 msec wide. Draw the circuit diagram. Determine the value of external component R_A if $C=1\ \mu F$ **04**
 (c) Compare RTD and Thermocouple. **03**
- OR**
- Q.4** (a) Draw the block diagram of 8051 microcontroller. Explain each block briefly. **07**
 (b) Differentiate between microprocessor and microcontroller. **04**
 (c) Explain Read Only Memory (ROM) **03**
- Q.5** Write a short note. (ANY TWO) **14**
 (a) Linear Variable differential Transformer (LVDT)
 (b) Phase measurement with the help of the Lissajous figures.
 (c) Successive Approximation Analog –To- Digital conversion.
 (d) 1) I-Pod 2) RFID.
