

GUJARAT TECHNOLOGICAL UNIVERSITY
B E Sem-VI Examination May 2011

Subject code: 160902
Date: 17/05/2011

Subject Name: Power Electronics-II
Time: 10.30 am – 01.00 pm
Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain half bridge and full bridge topology of inverter. **07**
(b) Explain 3 phase inverter operation for 180° . **07**
- Q.2** (a) Give comparison between current source inverter and voltage source inverter. **07**
(b) What is PWM? Explain SPWM techniques. **07**
- OR**
- (b) Explain space vector pulse modulation techniques. **07**
- Q.3** (a) Explain inverter operation for 120° . **07**
(b) Explain basic principle of cyclo-converter with circuit diagram and wave form? **07**
- OR**
- Q.3** (a) Explain three phase to single phase cycloconverter. **07**
(b) Explain the basics of Matrix converter. **07**
- Q.4** (a) Give the comparison between On/Off control and phase control of A.C voltage controller. **07**
(b) Explain full wave controller with R-L load. Draw the necessary wave-form. **07**
- OR**
- Q.4** (a) Explain slip-power recovery by Static Scherbius method for speed control of induction motor. **07**
(b) Explain application of converter in HVDC transmission. **07**
- Q.5** (a) Explain V/f control of induction motor drives? Give its merits and demerits. **07**
(b) Explain the method of rotor resistance control using static device for wound rotor motor. **07**
- OR**
- Q.5** (a) Explain the stator voltage control of induction motor drives. **07**
(b) Explain McMurray inverter with each mode of operation. Give its limitation. **07**
