

GUJARAT TECHNOLOGICAL UNIVERSITY

B E Sem-VI Examination May 2011

Subject code: 160905
Date: 23/05/2011

Subject Name: Electrical & Electronic Measurement
Time: 10.30 am – 01.00 pm
Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Classified error with their remedies. **07**
 (b) Explain Maxwell's bridge for measurement of self inductance. **07**

- Q.2** (a) Derive equation for De sauty's bridge for capacitor measurement with diagram. **07**
 (b) Explain Schering Bridge with diagram **07**

OR

- (b) Explain Campbell's bridge. **07**

- Q.3** (a) Which methods are used for the frequency measurement Explain any one. **07**
 (b) Limitation for the bridge measurement and their minimization **07**

OR

- Q.3** (a) Explain Anderson's bridge. **07**
 (b) Principal and working of digital LCR meter. **07**

- Q.4** (a) What are the problems with measurement of high resistance, Derive equation for measurement of insulation resistance. **07**
 (b) The four arms of bridge are as per given **07**
 Arm AB : capacitor C1 with internal resistor r1
 Arm BC: Non inductive resistance of R4=2000Ohm.
 Arm CD: Non inductive resistance of R3=2850Ohm
 Arm DA: capacitor C2= 0.5micro F, internal resistance r2=0.4Ohm and Resistor R2=4.8Ohm.
 Supply frequency 50hz between A and C and detector between B and D. For balance by above component. Find out capacitance C1 and internal resistor r1.

OR

- Q.4** (a) Explain construction features and working of flux meter **07**
 (b) Derive equation for ratio and phase angle error of a potential transformer. **07**

- Q.5** (a) Discuss the Varley loop test method for detection of cable fault. **07**
 (b) A single turn 200/5 Amp. C.T. has non-inductive burden of 1 Ohm. Magnetizing current is 80Amp. Calculate current ratio and phase angle of transformer. **07**

OR

- Q.5** (a) Explain construction and working of current transformer. **07**
 (b) Which methods are used for measurement of low resistance, Explain any one. **07**
