

GUJARAT TECHNOLOGICAL UNIVERSITY**B E Sem-VI Examination May 2011****Subject code: 162404****Subject Name: Industrial Drives & Control - I****Date: 21/05/2011****Time: 10.30 am To 1.00 pm****otal Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) List the advantages and disadvantages of thyristorised drives. **07**
(b) List various methods of speed control of dc shunt motor. Explain any two in detail **07**

- Q.2** (a) Derive the equation of the fundamental torque indicating dynamics of electric drives. **07**
(b) Explain Ward-Leonard system of dc drives with its advantages and disadvantages. **07**

OR

- (b) List the performance parameters of the dc drives. Define each of them. **07**

- Q.3** (a) Explain the speed control of a separately excited dc motor by a single-phase semi converter. Draw the voltage and current waveforms for continuous and discontinuous motor current. **07**
(b) Explain Dynamic and Composite braking of separately excited dc motor with chopper control. **07**

OR

- Q.3** (a) Explain forward motoring and braking control of separately excited dc motor using chopper control with waveforms. **07**
(b) Explain the working principle of ideal dual converter. Also explain the cosine firing control scheme. **07**

- Q.4** (a) Explain motoring operation of chopper controlled separately excited dc motor. **07**
(b) Derive the motor transfer function for separately excited dc motor. **07**

OR

- Q.4** (a) Explain Current Control Loop for separately excited dc motor drive. **07**
(b) Explain in detail the Phase Locked Loop control of the dc motor drive using block diagram. **07**

- Q.5** (a) Explain four quadrant variable speed drive employing a dual converter with non simultaneous control. **07**
(b) Explain the Microcomputer control of dc drives using block diagram. **07**

OR

- Q.5** (a) Explain semi converter operation of full converter for series dc motor drive with waveforms. **07**
(b) Explain the Servo Drives in Detail. **07**
