

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE SEM-VII Examination-Nov/Dec.-2011

Subject code: 170906

Date: 29/11/2011

Subject Name: Advance Power Electronics-I

Time: 10.30 am-01.00 pm

Total marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Assume suitable data, if necessary

- Q:1 (a) What is the necessity of Multi-level inverter? What are the advantages of it over single level inverter? 07
- (b) Explain half bridge and full bridge topology of inverter with wave form? 07

- Q-2 (a) Explain difference between multi pulse converter and multilevel converter with suitable diagram. 07
- (b) Explain the d.c voltage balance techniques for capacitor clamped multilevel inverter. 07

OR

- Q-2 (a) Explain diode clamped three level inverter with its switching table. 07
- (b) Give the comparison between all three configurations of multilevel inverter. 07

- Q-3 (a) Explain the zero voltage switched half bridge multi-resonant converter. 07
- (b) Explain parallel resonant inverter circuit with wave form. 07

OR

- Q-3 (a) Explain the H bridge topology for three level multilevel inverter with switching table. 07
- (b) Explain the buck converter with waveform. 07

- Q:4 (a) Explain operation of Fly-back converter with necessary wave-form 07
- (b) Explain the forward converter with waveform. Derive its output voltage expression. . 07

- Q-4 (a) Give the comparison between BLDC motor with Brushed D.C. motor and induction motor. 07
- (b) Which current control techniques are used for control of BLDC motor. Explain one of them very briefly. 07

OR

- Q-5 (a) Explain construction and working of switch reluctance motor. 07
- (b) Explain difference between sinusoidal and trapezoidal BLDC motor. 07

OR

- Q-5 (a) What is the difference between ON line UPS and OFF line UPS. 07
- (b) Explain the flying capacitor type multilevel inverter. 07
