

GUJARAT TECHNOLOGICAL UNIVERSITY
BE SEM-VII Examination-Nov/Dec.-2011

Subject code: 172403**Date: 24/11/2011****Subject Name: Power Processing Circuits-II****Time: 10.30 am-01.00 pm****Total marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) List and explain performance parameters of inverter. Explain the principle of operation of inverter using single-phase half bridge inverter with necessary waveforms. **07**
(b) Explain the Mc-Murray Bedford half bridge inverter with neat waveforms. **07**
- Q.2** (a) List the main drawbacks of controlled rectifiers. Explain the basics of active front- end rectifier. List the advantages of active front-end rectifier. **07**
(b) Explain the types of standby ac supply with block diagram. **07**
- OR**
- (b) List the types of batteries used for UPS. Explain the battery charging process in detail. **07**
- Q.3** (a) Explain sinusoidal pulse-width-modulation technique used for voltage control of single-phase inverters. **07**
(b) Explain phase dead-banding and draw the modulation reference waveforms for it. Explain triplen injection modulation. **07**
- OR**
- Q.3** (a) Explain the space vector with its representation. Explain the space vector sequence with waveforms. **07**
(b) Explain harmonic injected modulation and trapezoidal modulation with waveforms. **07**
- Q.4** (a) Give the comparison between 180° and 120° mode of conduction of 3-phase inverters. **07**
(b) Explain the single-phase multi level cascaded H-bridge inverter and its features. **07**
- OR**
- Q.4** (a) Explain M-type ZCS resonant converter with circuit diagram and waveforms. **07**
(b) Explain the principle of operation and features of flying capacitor 4-level bridge type multilevel inverter with necessary diagrams. **07**
- Q.5** (a) Explain integral cycle control with waveforms. Derive expressions for V_{or} , I_{Tr} and input power factor. **07**
(b) Explain the basic series resonant inverter with neat circuit and waveforms. Write the equations for design of series inverter. **07**
- OR**
- Q.5** (a) Explain the single-phase bidirectional controller having RL load with neat waveforms. **07**
(b) Explain the operation of bridge type single-phase to single-phase cycloconverter with continuous load current. Draw neat waveforms. **07**
