

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Semester -III Regular / Remedial Examination December - 2010****Subject code: 331101****Subject Name: Electronics Devices & Circuits-II****Date: 27 /12 /2010****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version Authentic

- Q.1** (a) Define the efficiency of a power amplifier and derive the formula for efficiency of class B push-pull amplifier **07**
 (b) Explain negative feedback and state the advantages of negative feedback. **07**
- Q.2** (a) Define the different types of Multi-vibrators and explain any one circuit with help of necessary waveforms. **07**
 (b) Explain the requirements for the oscillation and explain Hartley oscillator with the help of necessary circuit diagram. **07**
- OR**
- (b) Draw and explain the Wein-bridge oscillator circuit. **07**
- Q.3** (a) Compare common source, common gate and common drain amplifier using JFET. **07**
 (b) Explain characteristics and application of IGBT. **07**
- OR**
- Q.3** (a) Calculate voltage gain of FET amplifier having $g_m=5\text{mS}$ and $R_d=47\text{k}\Omega$ in common source configuration. Draw circuit with necessary biasing. **07**
 (b) Discuss the characteristics of Depletion and Enhancement types of MOSFET with their symbols and characteristic curve. **07**
- Q.4** (a) Explain the working operation with circuit diagram of following using Op-Amp. **07**
 (1) Summing Amplifier. (2) D to A converter.
 (b) Define the following parameters of Op-Amp and give their typical values for IC 741. **07**
 (1) CMRR (2) Slew rate (3) Gain Bandwidth product (4) Input bias current.
- OR**
- Q. 4** (a) Design the following using Op-Amp. **07**
 (1) Inverting amplifier with gain = 100.
 (2) Differentiator with time constant equal to 5 msec.
 (b) Comparison of JFET With MOSFET. **07**
- Q.5** (a) Explain the working of Schmitt Trigger circuit with neat sketch and waveform. **07**
 (b) Design the Monostable Multivibrator using IC-555 with on-time of 0.1 msec. **07**
- OR**
- Q.5** (a) Write short note **07**
 (1) Voltage Regulator. (2) Timer IC-555 Block Diagram.
 (b) Draw and explain circuit diagram of Current-series & Voltage-shunt type of feedback amplifier. **07**

- પ્રશ્ન-૧ અ પાવર એમ્પ્લિફાયર ની વ્યાખ્યા આપો અને ક્લાસ બી પુશ-પુલ પાવર એમ્પ્લિફાયર ની એફીસિયન્સી નું સુત્ર મેળવો. 07
- બ નેગેટિવ ફીડબેક સમજાવી અને તેના ફાયદા વર્ણવો . 07
- પ્રશ્ન-૨ અ મલ્ટી-વાઇબ્રેટર ના પ્રકારો ની વ્યાખ્યા આપો અને કોઇ પણ એક ની આકૃતિ અને વેવફોર્મ સાથે સમજાવો. 07
- બ ઓસીલેશન મેળવવા ની જરૂરીયાત સમજાવો અને આકૃતિ સાથે હાટૅલી ઓસીલેટર ને સમજાવો. 07
- અથવા
- બ વેઇન બ્રીઝ ઓસીલેટર ને આકૃતિ આપી સમજાવો. 07
- પ્રશ્ન-૩ અ કોમન સોર્સ , કોમન ગ્રાઉન્ડ અને કોમન ડ્રેઇન જે-ફેટ એમ્પ્લિફાયર ને સાથે સરખાવો. 07
- બ આઇ જી બી ટી ની લાક્ષણિકતા સમજાવો અને તેના ઉપયોગ વર્ણવો . 07
- અથવા
- પ્રશ્ન-૩ અ એફ ઇ ટી કોમન સોર્સ એમ્પ્લિફાયર ને $g_m=5mS$ અને $R_d=47k\Omega$ છે તો તેનો વોલ્ટેજ ગેઇન સોધો અને તેની જરૂરી બાયસિંગ સાથે આકૃતિ દોરો. 07
- બ ડીપ્લીશન અને એન્હાન્સમેન્ટ પ્રકારના મોસ-ફેટ તેના સીમ્બોલ સાથે સમજાવો. 07
- પ્રશ્ન-૪ અ ઓપેમ્પ એમ્પ્લિફાયર ની મદદ થી સમજાવો 07
1. સમીંગ એમ્પ્લિફાયર. 2. ડી ટુ એ કંવર્ટર.
- બ ઓપેમ્પ એમ્પ્લિફાયર IC 741 ના નીચેના પરીબળો ની વ્યાખ્યા આપો. 07
1. સિ. એમ આર આર 2. સ્લીવ રેઇટ.
3. ઇનપુટ બાયસ કરંટ 4. ગેઇન બેંડ વિથ પ્રોડક્ટ.
- અથવા
- પ્રશ્ન-૪ અ ઓપેમ્પ એમ્પ્લિફાયર ની મદદ થી ડીઝાઇન કરો. 07
1. ઇન્વર્ટિંગ એમ્પ્લિફાયર જેનો ગેઇન =100 હોય.
2. ડીફરન્સીયેટર સર્કિટ જેનો ટાઇમ કોન્સ્ટન્ટ =5 મિલી સેકન્ડ હોય
- બ જે-ફેટ અને મોસ-ફેટ ની સરખામણી કરો. 07
- પ્રશ્ન-૫ અ આકૃતિ સાથે સ્કેમીટ ટ્રીગર સમજાવો 07
- બ IC 555 ની મદદ થી મોનો સ્ટેબલ મલ્ટી-વાઇબ્રેટર ની ડીઝાઇન કરો જેનો ઓન-ટાઇમ 0.1 મિલી સેકન્ડ હોય. 07
- અથવા
- પ્રશ્ન-૫ અ ટ્રંક નોંધ લખો. 1. વોલ્ટેજ રેગ્યુલેટર. 2. ટાઇમર IC 555 નો બ્લોક ડાયાગ્રામ. 07
- બ કરંટ સીરીઝ અને વોલ્ટેજ સંટ પ્રકાર ના ફીડ-બેક એમ્પ્લિફાયર ને આકૃતિ દોરી સમજાવો. 07
