

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

Diploma Semester –Vth Examination December - 2010

Subject code: 352003

Subject Name: Programmable Logic Controllers

Date: 30 /12 /2010

Time: 02.30 pm – 05.00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- Q.1** (a) Explain Man and Machine Interface. 07
 (b) Note down Automation function and its objective. 07
Q.2 (a) Differentiate bipolar and unipolar stepper motor module. 07
 (b) Enlist the different types of timer and explain ON DELAY timer with timing diagram. 07

OR

- (b) Enlist the types of counter and explain any one with suitable example. 07
Q.3 (a) Draw the function block diagram of P.L.C. and explain it. 07
 (b) Explain parallel and serial data communication. 07

OR

- Q.3** (a) How we classify the processor ? why and when we need the latch ? 07
 (b) Explain P.L.C. scan cycle. 07
Q.4 (a) Draw the ladder diagram to operate four bulbs in series with constant time delay of 2sec. 07
 (b) Draw the ladder diagram to operate car parking house in following condition. 07
 1. On the green light and off the red light if car parking house has a space.
 2. On the red light and off the green light if car parking house has no space.
 3. The capacity of car parking house is 10 cars.

OR

- Q. 4** (a) Draw the function block diagram to operate counter as a digital clock. 07
 (b) Draw the function block diagram to operate following truth table. 07

I1	I2	I3	OUTPUT
1	0	0	Q1
0	1	0	
0	0	1	
1	1	0	Q2
0	1	1	
1	0	1	
1	1	1	Q3

- Q.5** (a) Draw the ladder diagram to operate water filling tank in following conditions. 07
 1. I1 switch to start the project.
 2. L1 sensor is upper sensor of tank.
 3. L2 sensor is lower sensor of tank.
 4. Q1 is an output given to solenoid.
 5. Following is a truth table to operate it.

L1	L2	Solenoid Output(Q1)
0	0	1
0	1	1
1	1	0
1	0	0 (Wrong condition)

- (b) Draw the latch diagram of I1 switch to operate output Q1 in both ladder as well as in function block diagram. Use I2 switch to break the latch in both diagram. **07**

OR

- Q.5** (a) Explain different types of logic used in P.L.C in ladder diagram **07**
(b) Explain discrete input-output module. **07**

પ્રશ્ન-૧ અ માણસ અને મશીન વચ્ચે નું જોડાણ સમજાવો. **07**

બ ઓટોમેસન ના સિદ્ધાન્ત અને હેતુઓ લખો. **07**

પ્રશ્ન-૨ અ ચુનિપોલાર અને બાયપોલાર સ્ટેપર મોટર વચ્ચે નો ભેદ સમજાવો. **07**

બ ટાઈમર ના વિવિધ પ્રકાર ના નામ આપો અને "ઓન ડિલે ટાઈમર" ટાઈમિંગ ડાયાગ્રામ સાથે સામજાવો. **07**

અથવા

બ કાઉન્ટર ના વિવિધ પ્રકાર ના નામ આપો અને તેમાનો એક પ્રકાર ઉદાહરણ સાથે સમજાવો. **07**

પ્રશ્ન-૩ અ પી.એલ.સી નો બ્લોક ડાયાગ્રામ દોરો અને સમજાવો. **07**

બ પેરેલલ અને સીરીયલ ડેટા કોમ્યુનિકેશન સમજાવો. **07**

અથવા

પ્રશ્ન-૩ અ પ્રોસેસર ને શેના આધારે જુદા પાડી શકાય ? પી. એલ. સી. મા કેમ અને ક્યારે લેટ્યુ વપરાય છે ? **07**

બ પી. એલ. સી. સ્કેન સાયકલ સમજાવો. **07**

પ્રશ્ન-૪ અ ચાર બટન ને ૨ સેકેન્ડ ના સમયાન્તરે એક પછી એક ચાલુ કરવા માટે નો લેડર ડાયાગ્રામ દોરો. **07**

બ નીચેની શરતો ને આધીન કાર પાર્કિંગ ઘર નો લેડર ડાયાગ્રામ દોરો. **07**

૧. જો કાર પાર્કિંગ ઘરમા જગ્યા હોય તો લીલી લાઈટ ચાલુ અને લાલા લાઈટ બંધ કરો.

૨. જો કાર પાર્કિંગ ઘરમા જગ્યા ના હોય તો લીલી લાઈટ બંધ અને લાલા લાઈટ ચાલુ કરો.

૩. કાર પાર્કિંગ ઘર ની ક્ષમતા ૧૦ કાર ની છે.

અથવા

પ્રશ્ન-૪ અ ફંક્શન બ્લોક ડાયાગ્રામ મા કાઉન્ટર નો ઉપયોગ કરી ડીઝીટલ ઘડિયાળ નો પ્રોગ્રામ બનવો. **07**

બ નીચેના ટ્રૂથ ટેબલ નો ફંક્શન બ્લોક ડાયાગ્રામ દોરો . **07**

આઈ ૧	આઈ ૨	આઈ ૩	આઉટપુટ
1	0	0	Q1
0	1	0	
0	0	1	
1	1	0	Q2
0	1	1	
1	0	1	

પ્રશ્ન-૫ અ નીચેની શરતો ને આધીન પાણીની ટાંકી ભરવા નો લેડર ડાયાગ્રામ દોરો. **07**

૧. આઈ૧ સ્વીચ પ્રોગ્રામ ચાલુ કરવા માટે.

૨. એલ ૧ સેન્સર ટાંકી ભરાઈ જાય તોજ ચાલુ થાય.

૩. એલ ૨ સેન્સર ટાંકી ખાલી હોય તોજ ચાલુ થાય.

૪. ક્યુ ૧ નળ ચાલુ કરવા માટે.

૫. નીચેના ટ્રૂથ ટેબલ પ્રમાણે તે કામ કરવો જોઈએ.

એલ ૧	એલ ૨	આઉટપુટ (Q1)
0	0	1
0	1	1
1	1	0
1	0	0

બ આઈ ૧ સ્વીચ ને લેટ્યુ કરી ક્યુ ૧ આઉટપુટ ચાલુ કરવા માટે નો લેડર તેમજ ફંક્શન બ્લોક ડાયાગ્રામ દોરો. **07**
લેટ્યુ તોડવા આઈ ૨ નો ઉપયોગ કરો.

અથવા

પ્રશ્ન-૫ અ પી. એલ. સી. મા વપરાતા જુદા-જુદા પ્રકાર ના લોજીક લેડર ડાયાગ્રામ ની મદદ વડે સમજાવો. **07**

બ ડીસ્ક્રીટ ઈનપુટ/આઉટપુટ મોડ્યુલ સમજાવો. **07**
