

Seat No: _____

Enrolment No: _____

GUJARAT TECHNOLOGICAL UNIVERSITY

Diploma Sem- II examination June-2009

Subject code: 320009

Subject Name: Electrical Circuit

Date: 25/6/2009

Time: 10.30 am to 1.00pm

Instructions:

Total Marks: 70

1. Attempt all questions
2. Make suitable assumptions wherever necessary
3. Figures to the right indicate full marks.

- Q.1** Explain the following questions in brief: **14**
- I Give limitations of ohm's law.
 - II Explain the term Permeability in magnetic circuit.
 - III Differentiate Dynamically and Statically induced e.m.f.
 - IV Three capacitors of $2\mu\text{f}$, $3\mu\text{f}$ and $6\mu\text{f}$ are connected in series across 250V dc supply. Find out the value of charge on each capacitor.
 - V An alternating current is represented by $i = 70.7 \sin(314t)$. Find out its Maximum value and RMS value.
 - VI Define power factor & state its values for pure resistive and pure inductive A.C. circuits.
 - VII State advantage of 3-phase system over single phase system.
- Q.2** (a) Prove that no power consumed in pure capacitor. **07**
(b) State and explain the Kirchoff's voltage law with suitable example. **07**
- OR**
- (b) Give comparison between Electrical circuit and Magnetic circuit. **07**
- Q.3** (a) Derive the expressions for converting delta connected network in to equivalent star connected network **05**
(b) State and explain Faraday's laws of electromagnetic induction. **05**
(c) Find out the value of current supplied by battery in network of **fig.1** **04**
- OR**
- Q.3** (a) Write short note on Hysteresis loop and state the information we are getting from that. **05**
(b) Derive the expression for co-efficient of coupling K between two coils. **05**
(c) A ring of 1 cm^2 cross sectional area, has cast steel for 100mm length and cast iron for 400mm length. Both the parts are separated by 1mm copper piece. A ring is wound with coil of 1500 turns. If flux density of 0.5 tesla is to be produced in ring, find out the value of current to be passed from coil. The relative permeability for cast steel and cast iron are 1100 & 300 respectively. **04**
- Q.4** (a) Define the coulomb's law and discuss the factors affecting it. **05**
(b) Derive the expression for charging voltage of capacitor. **05**
(c) Define: (1) Form factor (2) Peak factor (3) Phase (4) Phase difference **04**
- OR**
- Q.4** (a) Explain R-L series A.C. circuit with vector diagram and obtain equation of current **05**
(b) Explain the phenomenon of series resonance. Derive the expression for resonance frequency in series RLC circuit. **05**
(c) A 100Ω resistance is connected in series with inductance of 0.5 H. The series connection is given voltage $v = 400 \sin(314t + 45^\circ)$. Find out power factor and equation of current in circuit. **04**
- Q.5** (a) Explain active, reactive and apparent power with the help of power triangle. **05**

- (b) Q factor of parallel circuit. 05
(c) Vector $A = 25 + j10$, vector $B = 30 - j12$. find out A/B. 04

OR

- Q.5 (a) Explain the principle of generation of 3-phase voltage. Draw the waveform of 3-phase sinusoidal e.m.f. 05
(b) Derive the relation between line voltage and phase voltage in balanced three phase star system. 05
(c) Explain Admittance method for solving A.C. parallel circuit in brief. 04

સૂચના:

1. બધાજ પ્રશ્નોના જવાબ આપવા ફરજીયાત છે..
2. જરૂર જણાય ત્યાં યથા યોગ્ય ધારણાઓ બાંધવી.
3. જમણી બાજુ દર્શાવેલ આંકડા પ્રશ્નોના પૂરા ગુણ દર્શાવે છે.
4. પ્રશ્નપત્રની અંગ્રેજી પ્રત આધારભૂત ગણવી.

- પ્રશ્ન.૧ નીચેના પ્રશ્નોના ટૂંકમાં જવાબ આપો. 14
1. સોલ્ડમના નિયમની મર્યાદા ઓ જણાવો.
 2. મેગનેટીક સરકીટ માટે પરમીયાબીલીટી સમજાવો.
 3. ડાયનેમીકલી ઈન્ડયુસ ઈ.એમ.એફ અને સ્ટેટીકલી ઈન્ડયુસ ઈએમએફ વચ્ચેનો તફાવત જણાવો.
 4. ૨,૩, અને ૬ માર્ફકોફેરાડેના ત્રણ કેપેસિટર શ્રેણીમાં જોડીને ૨૫૦ વોલ્ટ ડી.સી. સપ્લાય સાથે જોડેલા છે તો દરેક કેપેસિટર ઉપરનો ચાર્જ શોધો
 5. એક પ્રત્યાવર્તી વિજ પ્રવાહનું સૂત્ર $i = 70.7 \sin(314t)$ છે. તો તેની મહત્તમ કિંમત અને RMS શોધો.
 6. પાવર ફેક્ટરની વ્યાખ્યા આપો. શુદ્ધ પ્રતિરોધ અને શુદ્ધ ઈન્ડક્ટરવાળી એ.સી. સરકીટ માટે તેની કિંમત જણાવો.
 7. થ્રી ફેસ પધ્ધતિના સીંગલ ફેસ પધ્ધતિ પરના ફાયદા જણાવો.
- પ્રશ્ન.૨ (અ) સાબિત કરો કે શુદ્ધ કેપેસિટર પરિપથમાં પાવરનું મુલ્ય શૂન્ય ઝેરૂં 07
(બ) કિર્ચોફના વોલ્ટેજનો નિયમ લખી ઉદાહરણ સાથે સમજાવો. 07
- અથવા
- પ્રશ્ન.૩ (બ) ઈલેક્ટ્રીક અને મેગનેટીક પરિપથની સરખામણી આપો. 07
(અ) ડેલ્થમાં જોડેલા નેટવર્કને તેના સમતુલ્ય સ્ટારમાં જોડેલ નેટવર્કમાં ફેરવવા માટેના સૂત્ર મેળવો. 05
(બ) ઈલેક્ટ્રોમેગનેટીક ઈન્ડક્શન અંગે ફેરાડેના નિયમો લખી સમજાવો. 04
(ક) આકૃતિ -૧ માં દર્શાવેલ નેટવર્કમાં બેટરી દ્વારા અપાતો વિજપ્રવાહ શોધો 04
- અથવા
- પ્રશ્ન.૩ (અ) “હિસ્ટરેસીસ લુપ” અંગે ટૂંકનોંધ લખો અને તેના દ્વારા કઈ માહિતી મળે છે તે જણાવો. 05
(બ) બે કોઈલ વચ્ચેના કપલીંગ કો-એફિસિયન્ટ “કે” નું સૂત્ર મેળવો. 05
(ક) 1 cm^2 આડછેદના શ્રેત્રફળવાળી રીંગમાં ૧૦૦ મી.મી ની લંબાઈ માટે કાસ્ટસ્ટીલ છે અને ૪૦૦ એમ.એમ લંબાઈ માટે કાસ્ટ આયર્ન છે. બન્ને ભાગો ૧ એમ.એમ કોપરના પીસથી જુદા પાડવાના આવેલ છે. રીંગ પર ૧૫૦૦ આંટાવાળી કોઈલ વીટવામાં આવેલ છે. જો રીંગમાં ૦.૫ ટેસલાની ફ્લક્સ ડેન્સિટી ઉત્પન્ન કરવી હોય તો કોઈલમાંથી કેટલો પ્રવાહ પસાર કરવો પડશે તે શોધો. કાસ્ટ સ્ટીલ તથા કાસ્ટ આયર્નની રીલેટીવ પર્મીયાબીલીટી અનુક્રમે ૧૧૦૦ તથા ૩૦૦ છે. 04
- પ્રશ્ન.૪ (અ) કુલંબને નિયમ લખો અને તેને અસર કરતા પરિબળો ચર્ચો 05
(બ) કેપેસિટરના ચાર્જીંગ વોલ્ટેજ માટેનું સૂત્ર મેળવો. 05
(ક) વ્યાખ્યા આપો. ૧. ફોર્મ ફેક્ટર ૨. પીક ફેક્ટર ૩. ફેઝ ૪. ફેઝ ડીફરન્સ 04
- અથવા
- પ્રશ્ન-૪ (અ) R-L series એ.સી સરકીટ વેક્ટર ડાયાગ્રામ સાથે સમજાવો. અને તેના વિજપ્રવાહનું સૂત્ર મેળવો 05
(બ) “શ્રેણીઅનુનાદ સમજાવો. RLC સીરીઝ સરકીટ માટે અનુનાદ આકૃતિ માટેનું સૂત્ર મેળવો. 05

- (ક) 100Ω પ્રતિરોધની સાથે 0.5 H ના ઈન્ડક્ટરને સીરીઝમાં જોડવામાં આવે છે. જોડાણને આપવામાં આવતા વોલ્ટેજને $v = 400\sin(314t + 45^\circ)$ થી દર્શાવવામાં આવે છે. તો પાવર ફેક્ટર અને સરકીટના વિજપ્રવાહનું સૂત્ર શોધો. **04**
- પ્રશ્ન-૫** (અ) એકટીવ, રીએકટીવ અને એપરેન્ટ પાવર પાવર ટ્રાયગલની મદદથી સમજાવો. **05**
- (બ) પેરેલલ સરકીટ માટે Q ફેક્ટર **05**
- (ક) વેક્ટર $A = 25 + j10$ અને વેક્ટર $B = 30 - j12$ તો A/B શોધો **04**
- અથવા**
- પ્રશ્ન-૫** (અ) થ્રી ફેઝ વોલ્ટેજના જનરેશનનો સિધ્ધાંત સમજાવો અને થ્રી ફેઝ સાયનુંસોયકલ ઈ.એમ.એફ ના વેવફોર્મ દોરો **05**
- (બ) થ્રી ફેઝ સ્ટાર જોડાણ માટે લાઈન વોલ્ટેજ તથા ફેઝ વોલ્ટેજ વચ્ચેનો સંબંધ દર્શાવતા સૂત્ર મેળવો. **05**
- (ક) એ.સી. પેરેલલ સરકીટ ઉકેલવા માટે એડમીટન્સની રીત ટૂંકમાં સમજાવો. **04**

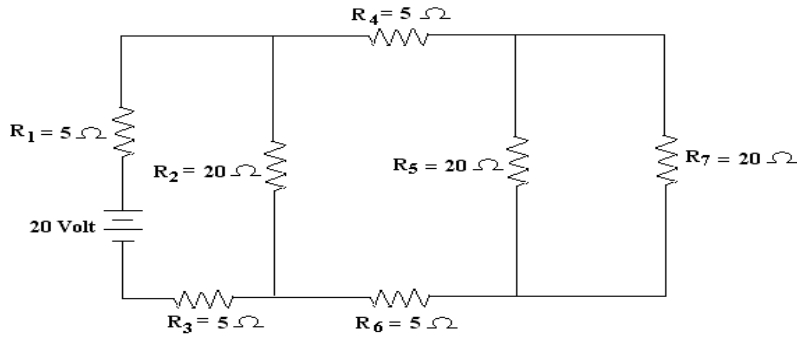


Fig.1
