

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Semester -III Examination January- 2010****Subject code: 331103****Subject Name: Electronics network and lines****Date: 27 / 01 / 2010****Time: 11.00 am – 1.30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic
5. Use of Programmable Calculator is strictly prohibited.

- Q.1** (a) Define: Branch, Characteristic impedance, VSWR, Reflection coefficient, Resonance, Cut off frequency, equalizer. **07**
(b) State and prove maximum power transfer theorem. **07**

- Q.2** (a) Define and explain quality factor and derive the equations for the same for inductor and capacitor. **07**
(b) Derive equations to convert T-type network into π -type network. **07**

OR

- (b) A circuit has a coil with $R=10\Omega$ and $L=0.2H$ is in parallel with a $C=2\mu F$. Determine the frequency of resonance, BW and Q for this circuit. **07**

- Q.3** (a) Derive the design equations for symmetrical T-network attenuator having load impedance R_o . **07**
(b) Explain constant-k type low pass filter with the help of necessary circuit diagram and derivation. **07**

OR

- Q.3** (a) Define attenuator .Give classification of different types of attenuators and uses of attenuator. **07**
(b) Design T-section m-derived low pass filter having cutoff frequency at 1000Hz, the frequency of infinite attenuation is 1065Hz and has characteristic impedance of 500Ω . **07**

- Q.4** (a) Derive the general line equations for voltage and current at any point on transmission line. **07**
(b) Derive the equation of characteristic impedance for symmetrical T-network. **07**

OR

- Q.4** (a) Explain the different types of distortions on a transmission line. **07**
(b) Compare active filter with passive filter. **07**

- Q.5** (a) Explain loading of telephone cable. **07**
(b) Explain mesh circuit analysis and node circuit analysis. **07**

OR

- Q.5** (a) Explain iron core transformer with the help of necessary derivation. **07**
(b) State and prove thevenin's theorem. **07**

- પ્રશ્ન-૧ અ વ્યાખ્યા લખો: બ્રાંચ, લાક્ષણિક પ્રતિબાધ, વી.એસ.ડબલ્યુ.આર., રીફ્લેક્શન કોએફિશિયન્ટ, ૦૭
અનુનાદ, કટ ઓફ ફિક્વન્સી, ઇક્વલાઇઝર.
- બ મેક્ષીમમ પાવર ટ્રાન્સફર થિયેરમ લખો અને સાબિત કરો. ૦૭
- પ્રશ્ન-૨ અ ક્વોલીટી ફેક્ટરની વ્યાખ્યા લખો અને સમજાવો તથા તેના માટેના સૂત્રો ઇન્ડક્ટર અને ૦૭
કેપેસિટર માટે મેળવો.
- બ ટી પ્રકારના નેટવર્કને પાઇ પ્રકારના નેટવર્કમાં ફેરવવા માટેના સૂત્રો મેળવો. ૦૭
- અથવા
- બ સર્કિટમાં $R=10$ ઓહમ અને $L=0.2$ હેન્રીની કોઇલ એ $C=2$ માઇક્રોફેરાડ સાથે ૦૭
સમાંતરમાં છે. આ સર્કિટ માટે રેઝોનન્ટ ફિક્વન્સી, બેન્ડવીથ તથા ક્યુ નક્કી કરો.
- પ્રશ્ન-૩ અ સીમેટ્રીકલ ટી નેટવર્ક એટેન્યુએટર કે જેનો લોડ પ્રતિબાધ R_0 હોય તેને માટે ડીઝાઇન ૦૭
સૂત્રો મેળવો.
- બ જરૂરી પરિપથ આકૃતિ તથા ડેરિવેશન દ્વારા કોન્સ્ટન્ટ કે પ્રકારનું લો પાસ ફિલ્ટર ૦૭
સમજાવો.
- અથવા
- પ્રશ્ન-૩ અ એટેન્યુએટરની વ્યાખ્યા આપો. વિવિધ પ્રકારના એટેન્યુએટર્સનું વર્ગીકરણ કરો અને ૦૭
એટેન્યુએટરના ઉપયોગો લખો.
- બ જેની કાપ આવૃત્તિ ૧૦૦૦ હર્ટ્ઝ, અગાધ એટેન્યુએશન માટેની આવૃત્તિ ૧૦૬૫ હર્ટ્ઝ ૦૭
અને લાક્ષણિક પ્રતિબાધ ૫૦૦ ઓહમ હોય તેવા ટી-સેક્શન એમ ડીરાઇવ્ઝ લો પાસ
ફિલ્ટરની રચના કરો.
- પ્રશ્ન-૪ અ ટ્રાન્સમિશન લાઇન પર કોઇ પણ બિંદુઓ પર વોલ્ટેજ તથા કરન્ટ માટેના સામાન્ય ૦૭
લાઇન સૂત્રો મેળવો.
- બ સમતુલિત ટી જાળપથ માટે તેના લાક્ષણિક પ્રતિબાધનું સૂત્ર મેળવો. ૦૭
- અથવા
- પ્રશ્ન-૪ અ પ્રસારણ લાઇન ઉપર જુદા જુદા પ્રકારના ડીસ્ટોર્સન્સ સમજાવો. ૦૭
- બ એક્ટીવ ફિલ્ટરને પેસિવ ફિલ્ટર સાથે સરખાવો. ૦૭
- પ્રશ્ન-૫ અ ટેલિફોન કેબલ પર લોડિંગ અસર સમજાવો. ૦૭
- બ નોડ પરિપથ પૃથ્થકરણ અને મેસ પરિપથ પૃથ્થકરણ સમજાવો. ૦૭
- અથવા
- પ્રશ્ન-૫ અ જરૂરી ડેરિવેશન દ્વારા આયર્ન કોર ટ્રાન્સફોર્મર સમજાવો. ૦૭
- બ થેવેનીન થિયેરમ લખો અને સાબિત કરો. ૦૭
