

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering Semester –VI Examination Dec. - 2011

Subject code: 360906

Date: 09/12/2011

Subject Name: Power Electronics

Time: 02.30 pm – 05.00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered Authentic.

- Q 1 (a) Explain speed control of universal motor using SCR. 7
(b) What are the different ways of controlling Induction Motor using SCRs. 7
Explain any one in brief.
- Q 2 (a) What are the different types of Cycloconverters? 7
(b) Write short note on LASCR. 7
OR
(b) Draw block diagram of UPS and explain major parts in it. 7
- Q 3 (a) Explain parallel inverter using SCR. 7
(b) What are the different types of Choppers? 7
Explain them in brief along with simple circuits.
OR
- Q 3 (a) Draw and explain John's Chopper circuit. 7
(b) Explain forced commutation of SCR. 7
- Q 4 (a) Write short note on Protection of SCRs. 7
(b) Compare inverter circuits using SCRs and Transistors. 7
OR
- Q 4 (a) Explain PWM method used in inverters. 7
(b) Draw block diagram of Robotics system, explain major parts in it. 7
- Q 5 (a) Explain operation of UJT along with its applications. 7
(b) Explain in detail operation of Triac with its symbol and construction. 7
OR
- Q 5 (a) Explain use of SCR in furnace temperature control. 7
(b) Explain the function of free wheeling diode. 7
-

- Q1 (a) યુનિવર્સલ મોટર નો SCR ની મદદ થી થતો સ્પીડ કંટ્રોલ સમજાવો. 7
(b) ઈંડક્શન મોટર ને SCR ની મદદ થી કંટ્રોલ કરવા માટેની રીતો સમજાઓ.
કોઈ પણ એક રીત ને વિગત વાર સમજાવો. 7
- Q2 (a) સાયકલોકન્વર્ટર ના પ્રકારો જણાવો. 7
(b) LASCR વીશે ટુંક નોંધ લખો. 7
અથવા
(b) UPS ની ખંડાકૃતિ દોરી મુખ્ય ભાગો સમજાવો. 7
- Q3 (a) SCR નો ઉપયોગ કરી પેરેલેલ ઈનવર્ટર સમજાવો. 7
(b) ચોપર ના પ્રકારો જણાવી, સર્કીટ દ્વારા ટુંક માં સમજાવો. 7
અથવા
(a) જોન્ ચોપર ની સરકીટ દોરી સમજાવો. 7
(b) SCR મા ફોર્સ કોમ્યુટેશન સમજાવો. 7
- Q 4 (a) SCR ના પ્રોટેક્શન વીશે ટુંક નોંધ લખો. 7
(b) SCR તેમજ ટ્રાંજિસ્ટર નો ઉપયોગ કરતા ઈનવર્ટર ની સરખામણી કરો. 7
અથવા
(a) ઈનવર્ટર મા વપરાતી PWM રીત સમજાવો. 7
(b) રોબોટીક સીસ્ટમ ની ખંડાકૃતિ દોરી મુખ્ય ભાગો સમજાવો. 7
- Q 5 (a) UJT ની કાર્યપ્રણાલી તેમજ ઉપયોગો દર્શાવો. 7
(b) ટ્રાયેક નુ ચિન્હ દોરો અને તેની કાર્યપ્રણાલી તેમજ બંધારણ સમજાવો. 7
અથવા
(a) ભઠ્ઠી ના તાપમાન નિયંત્રણ માટે SCR નો ઉપયોગ સમજાવો. 7
(b) ફી વ્હીલિંગ ડાયોડ નું કાર્ય સમજાવો. 7
-