

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

DIPLOMA - 1ST / 2ND SEMESTER-EXAMINATION –JUNE/JULY- 2012

Subject code: 310033

Subject Name: Fundamentals of Electronic

Date: 16/06/2012

Time: 10.30 am – 01.00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic

Q.1	(a)	Explain construction and working of PN junction diode.	07
	(b)	Compare CE CB and CC configuration for NPN transistor	07
Q.2	(a)	What is rectifier and explain any one with necessary circuit and waveforms.	07
	(b)	What is the need of the filter circuit? Explain any one filter circuit	07
		OR	
	(b)	Explain construction & working of electromagnetic relay.	07
Q.3	(a)	Explain N type and P type semiconductor materials.	07
	(b)	What is an amplifier? How transistor can be work as an amplifier	07
		OR	
Q.3	(a)	Draw & Explain construction, characteristics and applications of following (i) LED (ii) Photo transistor	07
	(b)	What is Oscillator. Explain any one in detail.	07
Q.4	(a)	What is transducer? Classify them.	07
	(b)	Explain ultrasonic flow detector.	07
		OR	
Q. 4	(a)	Why coupling is required? List the different types of coupling method and explain any one of them	07
	(b)	Explain the block diagram of CRO.	07
Q.5	(a)	Draw the symbol and characteristic of following devices.	14
		(a) Photo Diode (b) SCR (c) TRIAC (d) Zener Diode (e) UJT (f) DIAC (g) LDR	
		OR	
Q.5	(a)	Explain speed control of DC motor using SCR	07
	(b)	Explain smoke detector circuit.	07

પ્રશ્ન-1	(અ) PN જંક્શન ડાયોડનું કન્સ્ટ્રક્શન અને કાર્ય સમજાવો.	07
	(બ) CE, CB અને CC ટ્રાન્ઝિસ્ટર કન્ફિગ્યુરેશનની સરખામણી લખો.	07
પ્રશ્ન-2	(અ) રેક્ટીફાયર એટલે શું અને કોઈ પણ એક રેક્ટીફાયર સર્કિટ તરંગો સાથે સમજાવો	07
	(બ) ફિલ્ટરની આવશ્યકતા જણાવો અને કોઈ પણ એક ફિલ્ટર સર્કિટ સમજાવો.	07
	અથવા	
	(બ) ઇલેક્ટ્રોમેગ્નેટિક રિલેનું કન્સ્ટ્રક્શન અને કાર્ય સમજાવો.	07
પ્રશ્ન-3	(અ) N અને P પ્રકારના સેમિકન્ડક્ટર પદાર્થ સમજાવો.	07
	(બ) એમ્પલીફાયર એટલે શું? ટ્રાન્ઝિસ્ટર એમ્પલીફાયર તરીકે કેવી રીતે કાર્ય કરે છે?.	07
	અથવા	
પ્રશ્ન-3	(અ) નીચે મુજબના ડિવાઈસનું કન્સ્ટ્રક્શન, લાક્ષણિકતા અને એપ્લિકેશન જણાવો	07
	(a) LED (b) ફોટો ટ્રાન્ઝિસ્ટર	
	(બ) ઓસિલેટર એટલે શું.? કોઈ પણ એક વિગતવાર સમજાવો.	07
પ્રશ્ન-4	(અ) ટ્રાન્સડયૂસર એટલે શું? વર્ગીકરણ લખો	07
	(બ) અલ્ટ્રાસોનિક ફ્લો ડીટેક્ટર પર ટૂંક નોંધ લખો.	07
	અથવા	
પ્રશ્ન-4	(અ) કપલીંગની આવશ્યકતા જણાવો. કપલીંગના પ્રકારો લખો અને કોઈ એક સમજાવો.	07
	(બ) CROનો બ્લોક ડાયગ્રામ સમજાવો.	07
પ્રશ્ન-5	નીચે મુજબના ડિવાઈસની સંજ્ઞા અને લાક્ષણિકતા જણાવો	14
	(a) ફોટો ડાયોડ (b) SCR (c) TRIAC (d) ઝીનર ડાયોડ	
	(e) UJT (f) DIAC (g) LDR	
	અથવા	
પ્રશ્ન-5	(અ) ડીસી મોટરની સ્પીડ નિયંત્રણ કરવાનું કાર્ય SCR ની મદદથી સમજાવો.	07
	(બ) સ્મોક ડીટેક્ટર સર્કીટ સમજાવો.	07
