

GUJARAT TECHNOLOGICAL UNIVERSITY**DIPLOMA ENGG.- IIIrd SEMESTER-EXAMINATION – MAY/JUNE- 2012****Subject code: 330902****Date: 28/05/2012****Subject Name: Basic Electronics****Time: 02:30 pm – 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic

- Q.1** (a) Explain operation of CRT with necessary diagram. **07**
(b) Discuss Intrinsic and Extrinsic semiconductors with atomic structure & energy band diagram. **07**
- Q.2** (a) Explain working operation of semiconductor Diode with forward bias & reverse bias circuits and I-V characteristics. **07**
(b) Draw symbol, construction and characteristics curves of following devices: **07**
(i) Varactor diode.
(ii) Zener diode.
- OR**
- (b) Draw symbol, construction and characteristics curves of following devices: **07**
(i) TRIAC.
(ii) DIAC.
- Q.3** (a) Explain construction and basic operation of NPN transistor. **07**
(b) Define α and β of a transistor and derive relation between them. **07**
- OR**
- Q.3** (a) Explain transistor as an amplifier with CE configuration. **07**
(b) Define H- parameters of transistor. **07**
- Q.4** (a) Compare LED with semiconductor LASER diode. **07**
(b) Compare CE, CC and CB transistor amplifiers. **07**
- OR**
- Q. 4** (a) Explain construction and working operation of the following devices. **14**
(i) UJT.
(ii) SCR
- Q.5** (a) Explain construction and working operation of the following devices. **14**
(i) LED (ii) Photo diode.
- OR**
- Q.5** (a) Draw and explain application circuits of the following: **14**
(i) UJT (ii) TRIAC

પ્રશ્ન-૧	અ	જરૂરી ડાયગ્રામની મદદથી CRT ની કાર્યપદ્ધતિનું વર્ણન કરો.	07
	બ	ઇન્ટ્રીન્સીક અને એક્ષ્ટ્રીન્સીક સેમીકંડક્ટરની એટોમીક સ્ટ્રક્ચર અને એનર્જી બેન્ડ ડાયગ્રામ સાથે ચર્ચા કરો.	07
પ્રશ્ન-૨	અ	સેમી કંડક્ટર ડાયોડનું ફોરવર્ડ બાયસ, રીવર્સ બાયસ સર્કીટ અને I-V લાક્ષણિકતાની મદદથી વર્ણન કરો.	07
	બ	નીચેનાં કંપોનન્ટનાં સિમ્બોલ, બંધારણ અને લાક્ષણિકતા ગ્રાફ દોરો : (૧) વેરેક્ટર ડાયોડ (૨) ઝીનર ડાયોડ	07
		અથવા	
	બ	નીચેનાં કંપોનન્ટનાં સિમ્બોલ, બંધારણ અને લાક્ષણિકતા ગ્રાફ દોરો : (૧) ટ્રાયક (૨) ડાયક	07
પ્રશ્ન-૩	અ	એન પી એન ટ્રાંઝીસ્ટર નું બંધારણ અને મૂળભૂત કાર્ય પદ્ધતિ સમજાવો	07
	બ	ટ્રાંઝીસ્ટરના α અને β ની વ્યાખ્યા આપો અને તેમની વચ્ચેનો સંબંધ સાબીત કરો	07
		અથવા	
પ્રશ્ન-૩	અ	ટ્રાંઝીસ્ટરને એમ્પ્લીફાયર તરીકે CE સર્કીટ થી સમજાવો	07
	બ	ટ્રાંઝીસ્ટરના H પેરામીટરની વ્યાખ્યા આપો	07
પ્રશ્ન-૪	અ	LED ને સેમીકંડક્ટર LASER ડાયોડ સાથે સરખાવો	07
	બ	CE, CC અને CB ટ્રાંઝીસ્ટર એમ્પ્લીફાયરની સરખામણી કરો	07
		અથવા	
પ્રશ્ન-૪	અ	નીચેનાનું બંધારણ અને કાર્યપદ્ધતિ સમજાવો (1) UJT. (2) SCR	14
પ્રશ્ન-૫	અ	નીચેનાનું બંધારણ અને કાર્યપદ્ધતિ સમજાવો (i) LED (ii) Photo diode.	14
		અથવા	
પ્રશ્ન-૫	અ	નીચેનાની ઉપયોગી સર્કીટ દોરીને સમજાવો (i) UJT (ii) TRIAC	14
