

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGG.- IVth SEMESTER-EXAMINATION – JUNE- 2012

Subject code: 340901

Date: 18/06/2012

Subject Name: Fundamental of Electronics Circuits

Time: 02:30 pm – 05:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic

- Q.1** (a) Derive the equations of I_{dc} , E_{dc} , and I_{rms} for Full Wave Rectifier. **07**
(b) Explain the basic principle of SMPS. Draw the block diagram of SMPS and explain its working. **07**
- Q.2** (a) Draw and explain simple series voltage regulator and state its merits and demerits over zener regulator. **07**
(b) Draw the circuit of a feedback type series voltage regulator and explain its working. **07**
- OR**
- (b) Draw and explain Common Emitter Amplifier with its input and output waveforms. Define Voltage gain, Current gain and Power gain. **07**
- Q.3** (a) Explain in detail D.C. load line and the operating point. **07**
(b) Draw and explain potential divider type biasing circuit of transistor and obtain the value of its stability factor. **07**
- OR**
- Q.3** (a) Draw and explain the circuit of RC coupled amplifier. State its merits, demerits and applications. **07**
(b) State advantages and disadvantages of negative feedback in amplifier. Draw and explain the circuit of amplifier with negative feedback. **07**
- Q.4** (a) Draw the circuit of class B push-pull amplifier and explain its working. **07**
(b) Draw the circuit of RC phase shift oscillator and explain its working. State its advantages and disadvantages. **07**
- OR**
- Q. 4** (a) Explain the working of class A, B, AB and C amplifiers with waveforms. **07**
(b) Draw the circuit of Astable multivibrator using transistors and explain its working with waveforms. **07**
- Q.5** (a) Draw the circuit of Schmitt trigger using transistors and explain its working with waveforms. **07**
(b) Draw the functional block diagram of IC 555 and explain it. **07**
- OR**
- Q.5** (a) Draw the block diagram of digital multimeter and explain its working. **07**
(b) State the characteristics of an ideal OP-AMP. Draw and explain the block diagram of OP-AMP 741. Draw the symbol and show pin connections of OP-AMP 741. **07**

પ્રશ્ન-૧	અ	કુલવેવ રેક્ટિફાયર માટે Idc, Edc, અને Irms ના સૂત્ર મેળવો.	07
	બ	SMPS નો મુળભૂત સિધ્ધાંત સમજાવો. SMPS ની બ્લોક આકૃતિ દોરી કાર્ય સમજાવો.	07
પ્રશ્ન-૨	અ	સાદી સીરીઝ વોલ્ટેજ રેગ્યુલેટરની સરકીટ દોરી સમજાવો તેમજ તેના ઝીનર રેગ્યુલેટર પરના ફાયદા અને ગેરફાયદા જણાવો.	07
	બ	ફિડબેક પ્રકારના સીરીઝ વોલ્ટેજ રેગ્યુલેટરનો પરિપથ દોરી કાર્ય સમજાવો.	07
		અથવા	
	બ	કોમન એમીટર એમ્પ્લીફાયરનો પરિપથ દોરી ઇનપુટ અને આઉટપુટ વેવફોર્મ્સ સહિત સમજાવો. વોલ્ટેજ ગેઇન, કરંટ ગેઇન અને પાવર ગેઇનની વ્યાખ્યા આપો.	07
પ્રશ્ન-૩	અ	ડી.સી. લોડ લાઇન અને ઓપરેટીંગ પોઇન્ટ વિગતવાર સમજાવો.	07
	બ	ટ્રાન્ઝીસ્ટર બાયસીંગની પોટેન્શીયલ ડીવાઇડરની રીત આકૃતિ દોરી સમજાવો અને તેના સ્ટેબીલીટી ફેક્ટરની કિંમત મેળવો.	07
		અથવા	
પ્રશ્ન-૩	અ	RC કપલ્ડ એમ્પ્લીફાયરનો વીજ પરિપથ દોરી સમજાવો. તેના ફાયદાઓ, ગેરફાયદાઓ અને ઉપયોગો જણાવો.	07
	બ	એમ્પ્લીફાયરમાં નેગેટીવ ફીડબેકના ફાયદાઓ તેમજ ગેરફાયદાઓ જણાવો. નેગેટીવ ફીડબેક એમ્પ્લીફાયરનો વીજ પરિપથ દોરી સમજાવો.	07
પ્રશ્ન-૪	અ	વર્ગ B પુશપુલ એમ્પ્લીફાયરનો વીજ પરિપથ દોરો અને કાર્ય સમજાવો.	07
	બ	RC ફેઇઝ શીફ્ટ ઓસિલેટરનો પરિપથ દોરી કાર્ય સમજાવો. તેના ફાયદાઓ તેમજ ગેરફાયદાઓ જણાવો.	07
		અથવા	
પ્રશ્ન-૪	અ	એમ્પ્લીફાયર વર્ગ A, B, AB અને Cની કાર્યપ્રણાલી વેવફોર્મ્સ સહિત સમજાવો.	07
	બ	ટ્રાન્ઝીસ્ટરનો ઉપયોગ કરીને એસ્ટેબલ મલ્ટીવાઇબ્રેટરનો પરિપથ દોરી વેવફોર્મ્સ સહિત કાર્ય સમજાવો.	07
પ્રશ્ન-૫	અ	ટ્રાન્ઝીસ્ટરનો ઉપયોગ કરીને શ્મીટ ટ્રીગરનો પરિપથ દોરી વેવફોર્મ્સ સહિત કાર્ય સમજાવો.	07
	બ	IC 555 ની ફંક્શનલ બ્લોક આકૃતિ દોરીને સમજાવો.	07
		અથવા	
પ્રશ્ન-૫	અ	ડીજીટલ મલ્ટીમીટરની બ્લોક આકૃતિ દોરી કાર્ય સમજાવો.	07
	બ	આદર્શ OP-AMP ની લાક્ષણિકતાઓ જણાવો. OP-AMP 741 ની બ્લોક આકૃતિ દોરી સમજાવો. OP-AMP 741 નો સીમ્બોલ દોરી અને તેનાં પીન જોડાણો દર્શાવો.	07
