

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

DIPLOMA ENGG.- Vth SEMESTER-EXAMINATION – JUNE- 2012

Subject code: 350902/2350902

Date: 05/06/2012

Subject Name: Industrial Electronics

Time: 10:30 am – 01:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic

- Q.1** (a) Explain a SCR based speed control circuit for DC motor using armature control method. **07**
(b) Explain working of basic chopper circuit and state methods of voltage control in chopper. **07**

- Q.2** (a) State methods of commutation and explain any one method with appropriate diagram. **07**
(b) Explain construction, working and characteristics of IGBT. Also state its applications. **07**

OR

- (b) What is an inverter circuit. Explain the working of series inverter circuit with necessary waveforms. **07**
- Q.3** (a) State types of polyphase rectifier circuits. Explain a 3 phase full-wave bridge rectifier circuit with necessary waveforms. **07**
(b) Explain the construction, working and characteristics of SCR. **07**

OR

- Q.3** (a) Derive the values of I_{dc} and E_{dc} for 3 phase half-wave rectifier. **07**
(b) Explain pulse-control circuit for firing of SCR using UJT along with necessary waveforms. **07**

- Q.4** (a) Explain the principle of di-electric heating. Derive necessary equation for power loss and power density and state applications of di-electric heating. **07**
(b) Explain a line contactor circuit using SCR used in resistance welding. **07**

OR

- Q.4** (a) What is ultra-sonic waves (energy). List its applications and explain any one in detail. **07**
(b) What is energy-storage welding. Explain any one type of energy-storage welding. **07**

- Q.5** (a) Explain the principle of LDR. Explain a photo-relay circuit using LDR in which the relay operates when light beam is interrupted. **07**
(b) Explain the principle, construction and working of CVT with an appropriate diagram. **07**

OR

- Q.5** (a) Explain a photo-relay circuit using LASCR. **07**
(b) Explain the working of SMPS circuit with the help of block diagram. **07**

- પ્રશ્ન-૧** અ) આર્મેચર કન્ટ્રોલ પદ્ધતિથી ડી.સી.મોટરનાં ગતિ નિયંત્રણ માટે એસ.સી.આર. નાં ઉપયોગવાળો પરીપથ દોરીને સમજાવો. **07**

	બ	મૂળભૂત ચોપર પરીપથનું કાર્ય સમજાવો તથા તેના વોલ્ટેજ નિયંત્રણની રીતો જણાવો.	07
પ્રશ્ન-૨			
	અ	કોમ્યુટેશની જુદી રીતો જણાવો અને કોઈ પણ એક પદ્ધતિ યોગ્ય આકૃતિની મદદથી સમજાવો.	07
	બ	આય.જી.બી.ટી.નું બંધારણ,કાર્ય તથા લાક્ષણિકતા સમજાવો તથા તેની એપ્લીકેશન જણાવો.	07
		અથવા	
	બ	ઈન્વર્ટર એટલે શું ?સીરીસ ઈન્વર્ટર પરીપથનું કાર્ય સમજાવો યોગ્ય વેવફોર્મની મદદથી.	07
પ્રશ્ન-૩			
	અ	પોલીફેઝ રેક્ટીફાયર પરિપથનાં પ્રકાર જણાવો.૩-ફેઝ કુલ-વેવ બ્રિજ રેક્ટીફાયર પરીપથ સમજાવો યોગ્ય વેવ-ફોર્મની મદદથી,	07
	બ	એસ.સી.આર. નું બંધારણ,કાર્ય તથા લાક્ષણિકતા સમજાવો.	07
		અથવા	
પ્રશ્ન-૩			
	અ	૩-ફેઝ હાફ-વેવ રેક્ટીફાયર માટે Idc તથા Edc ની કિંમત તારવો.	07
	બ	એસ.સી.આર.નાં ફાયરીંગ માટે યુ.જે.ટી.નાં ઉપયોગ વાળો પલ્સ-કન્ટ્રોલ પરીપથ સમજાવો.	07
પ્રશ્ન-૪			
	અ	ડાયઇલેક્ટ્રીક હીટીંગનો સીધ્યાંત સમજાવો તથા પાવર-લોસ અને પાવર ડેન્સિટીનું સુત્ર તારવો તથા તેની એપ્લીકેશન જણાવો.	07
	બ	રેસીસટન્સ વેલ્ડીંગ માટે એસ.સી.આર.નો ઉપયોગ કરતો લાઈન-કોન્ટેક્ટર પરીપથ સમજાવો.	07
		અથવા	
પ્રશ્ન-૪			
	અ	અલ્ટ્રાસોનીક વેલ્ડ (એનર્જી) એટલે શું?તેની એપ્લીકેશન જણાવો તથા કોઈ પણ એક એપ્લીકેશન વિસ્તારથી સમજાવો.	07
	બ	એનર્જી-સ્ટોરેજ વેલ્ડીંગ એટલે શું?કોઈ પણ એક પ્રકારનો એનર્જી-સ્ટોરેજ વેલ્ડીંગ પરીપથ સમજાવો.	07
પ્રશ્ન-૫			
	અ	એલ.ડી.આર.નો સીધ્યાંત સમજાવો. એલ.ડી.આર.નો ઉપયોગ કરતો ફ્રોટો-રીલે પરીપથ સમજાવો જેમા પ્રકાશનું બીમ અવરોધાયે ત્યારે રીલે ઓપરેટ થાય.	07
	બ	સી.વી.ટી.નો સીધ્યાંત ,બંધારણ તથા કેવી રીતે કાર્ય કરે છે તે યોગ્ય આકૃતિની મદદથી સમજાવો.	07
		અથવા	
પ્રશ્ન-૫			
	અ	એલ.એ.એસ.સી.આર.નો ઉપયોગ કરતો ફ્રોટો-રીલે પરીપથ સમજાવો.	07
	બ	બ્લોક ડાટગ્રામની મદદથી એસ.એમ.પી.એસ. પરીપથનું કાર્ય સમજાવો.	07
