

GUJARAT TECHNOLOGICAL UNIVERSITY**DIPLOMA ENGG.- VIth SEMESTER-EXAMINATION – MAY/JUNE- 2012****Subject code: 360906/2360906****Date: 30/05/2012****Subject Name: Power Electronics****Time: 10:30 am – 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic

- Q : 1 (a) Draw the transistor analogy of S C R and explain its working. Write the applications of S C R. 07
- (b) Explain all four modes of operations in TRIAC. Draw and explain A C load control circuit using DIAC & TRAIC. 07
- Q : 2. (a) Draw Pulse Triggering circuit using P U T and explain its working. Write the advantages of P U T circuit over U J T circuit. 07
- (b) Draw the construction of I G B T, Explain its working. Write applications of I G B T . Write the advantages of I G B T over S C R. 07
- OR
- (b) What is commutation in S C R.? Explain any two forced commutation method in S C R. 07
- Q : 3. (a) Explain dv/dt ratings and di/dt ratings of S C R. 07
- (b) With necessary circuit diagram, Explain (i) Snubber Circuit (ii)Free wheeling diode for protection of S C R. 07
- OR
- Q : 3. (a) Explain the use of “ Heatsink “ with S C R and also explain its mounting. 07
- (b) Draw and explain working of MORGAN’S Chopper circuit. Write the application of Chopper. 07
- OR
- Q : 4. (a) Explain speed control of 3 Φ Slipring Induction Motor using d c chopper. 07
- (b) Draw and explain series inverter circuit using S C R and compare series inverter with parallel inverter. 07
- OR
- Q : 4. (a) What is P W M method? What are the advantages of P W M? Compare S C R inverter with Transistor inverter. 07
- (b) Draw the block diagram of U P S. Explain function of each block. Write the Application of U P S. 07
- Q : 5. (a) Explain basic principle of Cycloconverter. Draw and explain working of Single phase to Single phase Cycloconverter. 07
- (b) Draw and explain speed regulation circuit for D C Motor using armature voltage control method. 07
- OR
- Q : 5. (a) Draw and explain (I) Open Loop Control. (ii) Closed Loop Control For Universal Motor. 07
- (b) Draw block diagram of Robotics system and explain (I) Configuration of Robotics. (ii)Degree of freedom. 07

- પ્ર-૧ (અ) એસ.સી.આર. માટે ટ્રાન્સીસ્ટરની સામ્યતાનો પરિપથ દોરો અને તેનું કાર્ય સમજાવો. (૦૭)
એસ.સી.આર. ની ઉપયોગિતા લખો.
- (બ) ટ્રાયકના ચારે 'મોડ' નું કાર્ય સમજાવો. (૦૭)
ડાયક અને ટ્રાયકનો ઉપયોગ કરી એ.સી.લોડ કન્ટ્રોલનો પરિપથ દોરો અને સમજાવો
- પ્ર-૨ (અ) પી.યુ.ટી. નો ઉપયોગ કરી પલ્સ ટ્રીગરિંગ પરિપથ દોરો અને તેનું કાર્ય સમજાવો. (૦૭)
પી.યુ.ટી. પરિપથના યુ.જે.ટી. પરિપથ ઉપર ફાયદા લખો.
- (બ) આઈ.જી.બી.ટી. ના બંધારણની આકૃતિ દોરો તેનું કાર્ય સમજાવો. (૦૭)
આઈ.જી.બી.ટી. ની ઉપયોગિતા વર્ણવો.
આઈ.જી.બી.ટી. ના એસ.સી.આર ઉપર ફાયદા લખો.
- અથવા**
- (બ) એસ.સી.આર. માં કોમ્યુટેશન શું છે? (૦૭)
એસ.સી.આર. માટે ગમે તે 'બે' ફોર્સવાળા કોમ્યુટેશન વર્ણવો.
- પ્ર-૩ (અ) એસ.સી.આર. માટે ડીવી / ડીટી રેટીંગ્સ અને ડીઆઈ / ડીટી રેટીંગ સમજાવો (૦૭)
- (બ) એસ.સી.આર. ના પ્રોટેક્શન માટે જરૂરી પરીપથની આકૃતિ સાથે (૧) સ્નબર પરિપથ, (૨) ફ્રી વ્હીલીંગ ડાયોડ સમજાવો (૦૭)
- અથવા**
- પ્ર-૩ (અ) એસ.સી.આર. સાથે વપરાતી 'હીટસીક' વિષે સમજાવો અને તેના 'માઉન્ટીંગ' પણ સમજાવો. (૦૭)
- (બ) મોરગન ચોપરના પરિપથની આકૃતિ દોરી સમજાવો (૦૭)
ચોપરની ઉપયોગિતા લખો.
- પ્ર-૪ (અ) ડી.સી. ચોપરનો ઉપયોગ કરી થ્રી ફેસ ઇન્ડક્શન મોટરની ગતિ નિયંત્રણ નો પરિપથ દોરી સમજાવો. (૦૭)
- (બ) એસ.સી.આર. નો ઉપયોગ કરી સીરીઝ ઇન્વર્ટરનો પરિપથ દોરી સમજાવો. (૦૭)
સીરીઝ ઇન્વર્ટરને પેરેલલ ઇન્વર્ટર સાથે સરખાવો.
- અથવા**
- પ્ર-૪ (અ) પી.ડબલ્યુ.એમ. પદ્ધતિ શું છે? (૦૭)
પી.ડબલ્યુ.એમ. પદ્ધતિના ફાયદા શું છે? એસ.સી.આર ઇન્વર્ટરને ટ્રાન્સીસ્ટર ઇન્વર્ટર સાથે સરખાવો.
- (બ) યુ.પી.એસ. નો બ્લોક ડાયાગ્રામ દોરો. (૦૭)
દરેક બ્લોકનું કાર્ય સમજાવો.
યુ.પી.એસ.ની ઉપયોગિતા લખો
- પ્ર-૫ (અ) સાઈકલો કન્વર્ટરનો મૂળભૂત સિધ્ધાંત સમજાવો. સીંગલફેઝથી સીંગલફેઝ સાઈકલોકન્વર્ટરનો પરિપથ દોરી તેનું કાર્ય સમજાવો. (૦૭)
- (બ) આર્મચર વોલ્ટેજ કન્ટ્રોલ પદ્ધતિનો ઉપયોગ કરી ડી.સી.મોટર માટેની ગતિ નિયંત્રણ પરિપથ દોરી સમજાવો. (૦૭)
- અથવા**
- (અ) યુનિવર્સલ મોટર માટે (૧) ઓપનલુપ કન્ટ્રોલ (૨) કલોઝડ લુપ કન્ટ્રોલ પરિપથ દોરી સમજાવો. (૦૭)
- (બ) રોબોટીક પદ્ધતિનો બ્લોક ડાયાગ્રામ દોરો. (૦૭)
સમજાવો (૧) રોબોટીક્સના કન્ફ્યુગરેશન
(૨) ડીઝી ઓફ ફ્રીડમ
