

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

DIPLOMA ENGG.- VIth SEMESTER-EXAMINATION – MAY/JUNE- 2012

Subject code: 361702

Date: 28/05/2012

Subject Name: Industrial Electronics and Control

Time: 10:30 am – 01:00 pm

Total Marks: 70

Instructions:

- 1. Attempt all questions.**
- 2. Make suitable assumptions wherever necessary.**
- 3. Figures to the right indicate full marks.**
- 4. English version is considered to be Authentic**

- Q.1** (a) What do you mean by commutation of SCR? Explain the Class-C commutation method with the help of circuit diagram. **07**
- (b) Define and explain the following terms briefly in connection with SCR. **07**
(i) Latching current (ii) Holding current
- Q.2** (a) Enlist the various types of triggering methods of SCR. Explain any one of them in detail. **07**
- (b) With the help of circuit diagram, explain the two transistor analogy of an SCR. **07**
- OR**
- Q.3** (b) Draw the V-I characteristics of a TRIAC and explain its working principle. **07**
- (a) Draw and explain the equivalent circuit and V-I characteristics of the UJT in detail. **07**
- (b) Compare power MOSFET and power BJT. **07**
- OR**
- Q.3** (a) Explain the operation of IGBT with the help of neat structural diagram and suitable waveforms. **07**
- (b) Compare IGBT and power MOSFET. **07**
- Q.4** (a) Describe with a neat circuit diagram the basic principle of a dual converter. **07**
- (b) Develop a microprocessor based firing scheme for three phase fully controlled bridge circuit. **07**
- OR**
- Q. 4** (a) What is cyclo-converter? Explain single phase to single phase cyclo- converter circuit for bridge configuration. **07**
- (b) Classify thyristor inverter? Draw a circuit diagram of a parallel inverter using two SCRs and explain its working. **07**
- Q.5** (a) With the help of circuit diagram and output voltage waveforms, explain the principle of operation of a chopper **07**
- (b) Explain the various schemes of DC motor speed control **07**
- OR**
- Q.5** (a) Explain the necessity of energy storage welding. Explain capacitor type energy storage welding. **07**
- (b) Explain the resistance welding cycle. Explain electrical control circuit used in sequential timer for resistance welding process. **07**

પ્રશ્ન-૧	અ	એસ .સી. આર. કોમ્પ્યુટેશન એટલે શુ? ક્લાસ – સી કોમ્પ્યુટેશનની પદ્ધતિ પરીપથની મદદથી સમજાવો.	07
	બ	વ્યાખ્યા આપી ટુંકમાં વર્ણવો. (i) લેચિંગ પ્રવાહ (ii) હોલ્ડીંગ પ્રવાહ	07
પ્રશ્ન-૨	અ	એસ .સી. આર. ની વિવિધ ટ્રીગરીંગ પદ્ધતિઓના નામ જણાવો. કોઈ પણ એક પદ્ધતિનું વિસ્તૃત વર્ણન કરો.	07
	બ	એસ .સી. આર. નુ બે ટ્રાન્સિસ્ટર મોડેલ પરીપથની મદદથી સમજાવો.	07
		અથવા	
	બ	ટ્રાયેકની વોલ્ટેજ- પ્રવાહ ની લાક્ષણિકતા દોરી તેનો કાર્યસિદ્ધાંત સમજાવો.	07
પ્રશ્ન-૩	અ	યુ. જે. ટી. ની વોલ્ટેજ- પ્રવાહ ની લાક્ષણિકતા દોરી પરીપથની મદદથી સમજાવો.	07
	બ	પાવર મોસફેટ અને પાવર બીજેટી ની સરખામણી કરો.	07
		અથવા	
પ્રશ્ન-૩	અ	આઇ. જી. બી. ટી.નું ઓપરેશન સ્વચ્છ ડાયાગ્રામ અને યોગ્ય વેવફોર્મ સાથે વર્ણવો.	07
	બ	આઇ. જી. બી. ટી. અને પાવર મોસફેટ ની સરખામણી કરો.	07
પ્રશ્ન-૪	અ	ડયુઅલ કનવર્ટર નો કાર્યસિદ્ધાંત પરીપથની મદદથી સમજાવો.	07
	બ	થ્રી-ફેઝ કુલ્લી કંટ્રોલ્ડ બ્રીજ કનવર્ટર માટે માઇક્રોપ્રોસેસર આધારિત ફાયરીંગ સ્કીમ વિકસાવો.	07
		અથવા	
પ્રશ્ન-૪	અ	સાઇકલો- કનવર્ટર એટલે શુ? 1-ફેઝ થી 1-ફેઝ સાઇકલો- કનવર્ટર પરીપથની મદદથી સમજાવો.	07
	બ	થાઇરસ્ટર ઇનવર્ટરનું વર્ગીકરણ કરો. બે એસ .સી. આર. નો ઉપયોગ કરી સમાંતરીય ઇનવર્ટરની કાર્યરચના પરીપથની મદદથી સમજાવો.	07
પ્રશ્ન-૫	અ	ચોપર નો કાર્યસિદ્ધાંત પરીપથ અને આઉટપુટ વેવફોર્મની મદદથી સમજાવો.	07
	બ	ડી. સી. મોટર ના ગતિ નિયંત્રણ ની વિવિધ પદ્ધતિઓ વર્ણવો.	07
		અથવા	
પ્રશ્ન-૫	અ	ઉર્જા સંગ્રહ વેલ્ડીંગની જરૂરિયાત સમજાવો. કેપીસીટર પ્રકારનું ઉર્જા સંગ્રહ વેલ્ડીંગ વર્ણવો.	07
	બ	રેસીસ્ટીવ વેલ્ડીંગ ચક્ર વર્ણવો. રેસીસ્ટીવ વેલ્ડીંગ માટેના સિસ્કવેસિયલ ટાઇમરનો વિધ્યુત નિયંત્રણ પરીપથ સમજાવો.	07
