

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-III • EXAMINATION – SUMMER 2013****Subject Code: 331101****Date: 06-06-2013****Subject Name: Electronics Devices and Circuits-II****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- | | | |
|-------------|--|-----------|
| Q.1 | (a) What is negative feedback in amplifiers? Explain the effect of negative feedback on different parameters of amplifiers. | 07 |
| | (b) Design Wein bridge oscillator with 10Khz frequency. | 07 |
| Q.2 | (a) Explain Complementary symmetry push-pull amplifier. | 07 |
| | (b) Draw circuit diagram of Class A power amplifier with transformer coupled load and show that its maximum collector efficiency is 50%. | 07 |
| | OR | |
| | (b) Explain different types of distortion occur in power amplifiers. | 07 |
| Q.3 | (a) Design an astable multivibrator using transistor with 1Khz frequency and 50% duty cycle. | 07 |
| | (b) Draw the Schmitt trigger circuit and explain its working. Explain UTP and LTP. | 07 |
| | OR | |
| Q.3 | (a) Draw the circuit diagram of differentiating circuit and show that output voltage of differentiator is proportional to differentiaion of input voltage also draw the o/p waveforms for different type of input. | 07 |
| | (b) Draw and explain bistable multivibrator circuit using transistor. | 07 |
| Q.4 | (a) Explain construction and working of N-channel JFET. | 07 |
| | (b) Draw and explain working of common source amplifier circuit using JFET. | 07 |
| | OR | |
| Q. 4 | (a) Compare FET and BJT. | 07 |
| | (b) Explain the construction and working of Enhancement type MOSFET. | 07 |
| Q.5 | (a) Write the characteristics of Ideal op-amp and applications of op-amp. | 07 |
| | (b) Draw and explain functional block diagram of IC 555. | 07 |
| | OR | |
| Q.5 | (a) Draw pin diagram of IC 8038 and explain its working as waveform generator. | 07 |
| | (b) Draw and explain the difference amplifier (subtractor) using op-amp. | 07 |

- પ્ર.૧ (અ) એમ્પ્લીફાયમાં નેગેટીવ ફીડબેક શું છે? એમ્પ્લીફાયરના અલગ અલગ પેરામીટર પર તેની અસર સમજાવો. 07
- (બ) ૧૦ KHz આવૃત્તિવાળો વેન બ્રીજ ઓસીલેટર ડિઝાઇન કરો. 07
- પ્ર.૨ (અ) કોમ્પ્લીમેન્ટ્રી સીમેન્ટ્રી પુશ-પુલ એમ્પ્લીફાયર સમજાવો. 07
- (બ) ટ્રાંસફોર્મર કપલ્ડ વર્ગ-અ પાવર એમ્પ્લીફાયરની સર્કીટ દોરો અને બતાવો કે તેની મહત્તમ કાર્યક્ષમતા ૫૦% છે. 07

અથવા

- (બ) પાવર એમ્પ્લીફાયરમાં થતી અલગ-અલગ પ્રકારની વિકૃતિઓ સમજાવો. 07
- પ્ર.૩ (અ) ૧ KHz આવૃત્તિ અને ૫૦% ડ્યુટી સાયકલ વાળો એસ્ટેબલ મલ્ટીવાઇબ્રેટર ટ્રાંજીસ્ટર નો ઉપયોગ કરીને ડિઝાઇન કરો 07
- (બ) સ્ક્રીટ ટ્રીગર સર્કીટ દોરો અને તેનું કાર્ય સમજાવો તથા UTP અને LTP સમજાવો. 07

અથવા

- પ્ર.૩ (અ) ડીફ્રીસીંગ સર્કીટ દોરો અને બતાવો કે તેનું આઉટપુટ ઇનપુટના વિકલનના સમપ્રમાણમાં હોય છે. તથા અલગ અલગ પ્રકારના ઇનપુટ માટે આઉટપુટ વેવફોર્મ દોરો. 07
- (બ) ટ્રાંસિસ્ટરથી બનેલ બાઇસ્ટેબલ મલ્ટીવાઇબ્રેટરની સર્કીટ દોરો અને સમજાવો. 07
- પ્ર.૪ (અ) N-ચેનલ JFET નું બંધારણ અને કાર્ય સમજાવો. 07
- (બ) JFET થી બનેલ કોમન સોર્સ એમ્પ્લીફાયરની સર્કીટ દોરો અને તેનું કાર્ય સમજાવો. 07

અથવા

- પ્ર.૪ (અ) FET અને BJT ની સરખામણી કરો. 07
- (બ) એન્હાંસમેન્ટ પ્રકારના MOSFET નું બંધારણ અને કાર્ય સમજાવો. 07
- પ્ર.૫ (અ) આદર્શ op-amp ની ખાસિયત લખો તથા op-amp ના ઉપયોગો લખો. 07
- (બ) IC 555 ની કાર્યાત્મક ખંડાકૃતિ દોરો અને સમજાવો. 07

અથવા

- પ્ર.૫ (અ) IC 8038 નો પીન ડાયગ્રામ દોરો અને વેવફોર્મ જનરેટર તરીકે તેનું કાર્ય સમજાવો. 07
- (બ) op-amp નો ઉપયોગ કરીને બનાવેલ ડીફરેન્સ એમ્પ્લીફાયર દોરો અને સમજાવો.
