

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-IV • EXAMINATION – SUMMER 2013****Subject Code: 341103****Date: 07-06-2013****Subject Name: Industrial Electronics****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Draw the block diagram of open loop and closed loop control system and state difference between them. **07**
- (b) Explain servomechanism with the help of example. **07**
- Q.2** (a) With the help of two transistor analogy explain the working of SCR. **07**
- (b) Explain single phase full wave controlled rectifier with half controlled bridge. **07**
- OR**
- Q.3** (b) Draw and explain construction of UJT. **07**
- (a) State the advantages of poly phase rectifier. **07**
- (b) Draw the circuit of bridge type single phase cycloconverter and explain its working. **07**
- OR**
- Q.3** (a) State applications of poly phase rectifier. **07**
- (b) Explain three phase full wave bridge rectifier. Draw the necessary waveforms. **07**
- Q.4** (a) Draw and explain the circuit for the speed regulation of DC motor using techogenerator. **07**
- (b) Using two SCR connected back to back, explain how the speed control of single phase AC motor is obtained. **07**
- OR**
- Q. 4** (a) Explain Uninterrupted Power Supply. **07**
- (b) Explain principle of dielectric heating and state its application. **07**
- Q.5** (a) Explain the sequential timer using IC-555. **07**
- (b) Write about the source of biomedical potential. **07**
- OR**
- Q.5** (a) Draw the block diagram of PLC and explain the function of each block. **07**
- (b) Compare between induction and dielectric heating. **07**

પ્રસ્ન ૧	અ.	ઓપન લુપ અને ક્લોસડ લુપ સીસ્ટમનો બ્લોક ડાયાગ્રામ દોરો અને તેમની વચ્ચેનો તફાવત દર્શાવો .	૦૭
	બ.	કોઈ એક ઉદાહરણ ની મદદથી સર્વોમીકેનીઝમ સમજાવો.	૦૭
પ્રસ્ન ૨	અ.	બે ટ્રાન્સીસ્ટર સાથે સરખામણી કરીને એસ.સી.આર. વિશે સમજાવો.	૦૭
	બ.	હાફ કંટ્રોલ્ડ બ્રીઝ સાથેનો સીંગલ ફેઝ ફુલવેવ કંટ્રોલ્ડ રેક્ટીફાયર સમજાવો .	૦૭
અથવા			
	બ.	યુ. જે. ટી. દોરીને તેની કાર્ય પ્રણાલી સમજાવો.	૦૭
પ્રસ્ન ૩	અ.	પોલીફેઝ રેક્ટીફાયરના ફાયદાઓ લખો.	૦૭
	બ.	બ્રીઝ ટાઇપ સીંગલ ફેઝ સાયકલોકંવર્ટર દોરો અને તેની કાર્યપ્રણાલી સમજાવો.	૦૭
અથવા			
પ્રસ્ન ૩	અ.	પોલીફેઝ રેક્ટીફાયરની ઉપયોગીતાઓ લખો.	૦૭
	બ.	થ્રી ફેઝ ફુલ વેવ બ્રીઝ રેક્ટીફાયર્ સમજાવો અને તેના વેવફોર્મ	૦૭
પ્રસ્ન ૪	અ.	ડી.સી. મોટરનુ સ્પીડ રેગ્યુલેશન ટેકોજનરેટરથી દોરીને સમજાવો.	૦૭
	બ.	સીંગલ ફેઝ એ.સી. મોટરનો સ્પીડ કંટ્રોલ બે બેક ટુ બેક એસ.સી.આરની મદદથી સમજાવો.	૦૭
અથવા			
પ્રસ્ન ૪	અ.	યુ.પી.એસ. સમજાવો.	૦૭
	બ.	ડાઇ ઇલેક્ટ્રીક હીટીંગનો સિધ્ધાંત સમજાવો અને તેની ઉપયોગીતાઓ લખો.	૦૭
પ્રસ્ન ૫	અ.	આઇ.સી. 555 વાપરીને સીક્વન્સીયલ ટાઇમર સમજાવો.	૦૭
	બ.	બાયોમેડીકલ પોટેન્સીયલના સોર્સ વિશે જણાવો.	૦૭
અથવા			
પ્રસ્ન ૫	અ.	પી.એલ.સી. નો બ્લોક ડાયાગ્રામ દોરો અને દરેક બ્લોક સમજાવો.	૦૭
	બ.	ઇન્ફ્રશન હીટીંગ અને ડાઇ ઇલેક્ટ્રીક હીટીંગની સરખામણી કરો.	૦૭
