

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering - SEMESTER-IV • EXAMINATION – SUMMER 2013

Subject Code: 342402

Date: 10-06-2013

Subject Name: Electrical Networks and Circuits


Time: 10:30 am - 01:00 pm

Total Marks: 70


Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

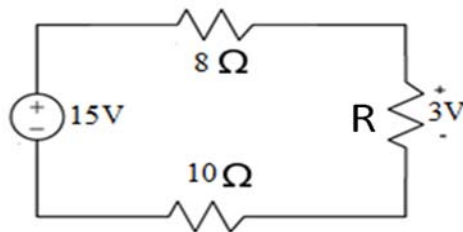
Q.1 (a) Define Kirchhoff's voltage law (KVL) and find out value of R in the given circuit. 07



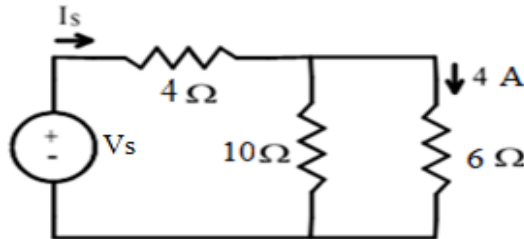(b) Define Kirchhoff's current law (KCL) and Determine I_s in the circuit below using Current divider rule. 07




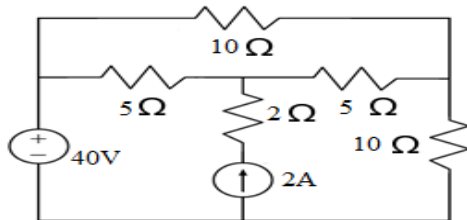Q.2 (a) Find out voltage across 2 ohm resistance using Nodal analysis. 07



07

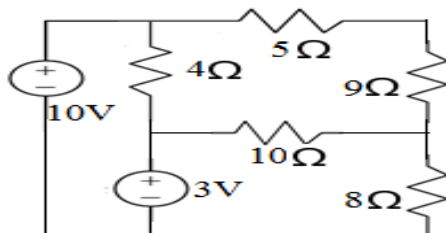(b) Find out current through 9 ohm resistance using Mess analysis. 07




OR

(b) Explain simple Nodal and Mess analysis technique for solving electrical circuits. 07


- Q.3** (a) Define Resonance. Explain series resonance in detail with impedance and current variation. **07**
 (b) Derive an equation of quality factor for R-L Series and R-C Series circuit. **07**

OR

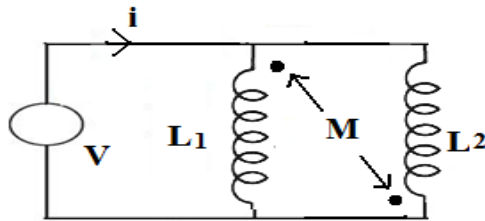- Q.3** (a) Derive an equation of total inductance for series connections of mutually coupled coils with necessary circuit diagrams. **07**
 (b) Find out equivalent inductance (L_{eq}) for the given mutually coupled coils ($L_1=30\text{mH}$, $L_2=50\text{mH}$, $M=2\text{mH}$)



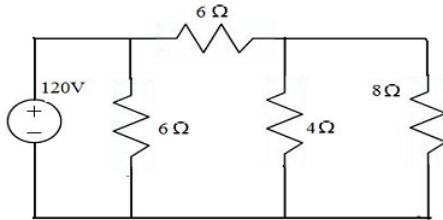
- Q.4** (a) Find out power dissipated by 8ohm resistance using Thevenin's Theorem. **07**



- (b) Derive condition for maximum power transfer in a D.C. circuit and also find out value of maximum power for the same circuit. **07**


OR

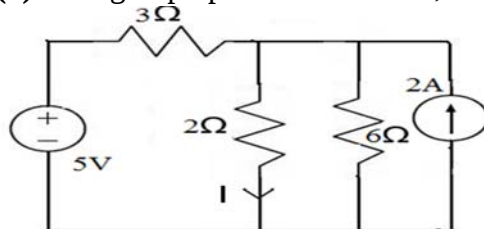- Q.4** (a) Using Superposition Theorem, find out current I through 2ohm resistance. **07**



- (b) Explain Millman's Theorem and Norton's theorem in Short. **07**

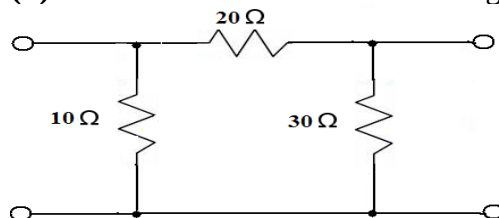- Q.5** (a) Determine open circuit impedance (Z) parameters of two port network **07**
 (b) Determine Y-Parameters for the given circuit.




OR

- Q.5** (a) Derive initial conditions in circuit element resistor, capacitor & inductor **07**
 (b) Derive Time response equation of series R-C circuit connected to a D.C. voltage source. **07**


પ્રશ્ન ૧ અ કિરચોફનો વોલ્ટેજ નો નિયમ વ્યાખ્યાયીત કરો અને આપેલી સર્કીટ માથી R ની કીમત શોધો.

07

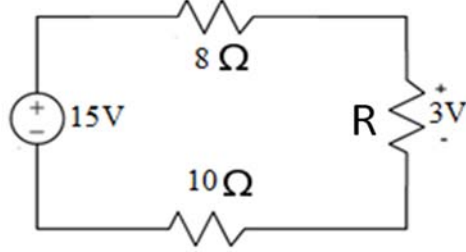


પ્રશ્ન ૧ બ કિરચોફ નો કરન્ટ નો નિયમ વ્યાખ્યાયીત કરો અને આપેલી સર્કીટ માથી કરન્ટ વિભાજન નિયમ ની મદદ થી I_S ની કીમત શોધો.

07

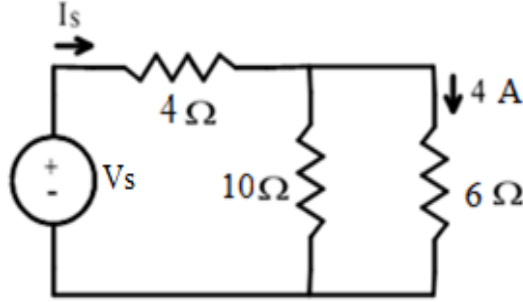


પ્રશ્ન ૨ અ નોડલ એનાલીસીસ ની મદદ થી 2 ઓહ્મ અવરોધ મા મળતા વોલ્ટેજ શોધો.

07

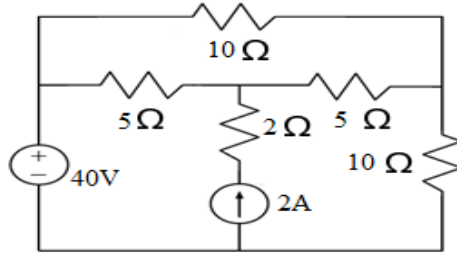

બ મેશ એનાલીસીસ ની મદદ થી 9 ઓહ્મ અવરોધ માથી પસાર થતો વિદ્યુત પ્રવાહ શોધો.

07

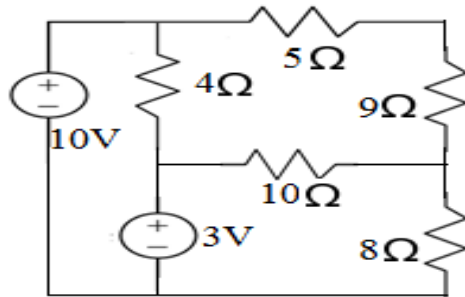

અથવા

બ સામાન્ય નોડલ અને મેશ એનાલીસીસ ની રીત ટુક મા વર્ણવો.

07


પ્રશ્ન ૩ અ રેઝોનન્સ વ્યાખ્યાયિત કરો અને સીરીઝ રેઝોનન્સ - ઇમ્પીડન્સ અને વિદ્યુત પ્રવાહ વેરિએશન સાથે વિસ્તાર મા વર્ણવો. 07

બ સીરીઝ R-L અને સીરીઝ R-C માટે ક્વોલીટી ફેક્ટર નુ સમીકરણ તારવો. 07


અથવા

પ્રશ્ન ૩ અ જરૂરી સરકીટ ડાયાગ્રામ સાથે મ્યુચ્યુલી કપલ્ડ કોઈલ ના સીરીઝ કનેક્શન માટે ના કુલ ઈંડક્ટન્સ માટે નુ સમીકરણ તારવો. 07

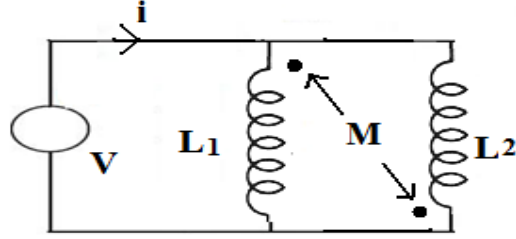બ આપેલ મ્યુચ્યુલી કપલ્ડ કોઈલ માટે કુલ સમાંતરીય ઈંડક્ટન્સ શોધો
($L_1=30\text{mH}$, $L_2=50\text{mH}$, $M=2\text{mH}$) 07



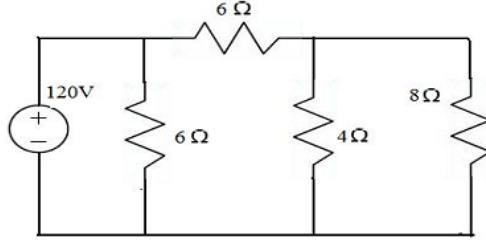
પ્રશ્ન ૪ અ થેવીનિન થીયરમ નો ઉપયોગ કરી ને ૪ ઓહ્મ અવરોધ માથી થતો પાવર નો વ્યય શોધો. 07



બ ડી.સી. સરકીટ મા મહત્તમ પાવર ટ્રાન્સફર કરવા માટે ની શરત તારવો. અને મહત્તમ પાવર ની કીમત શોધો. 07

અથવા

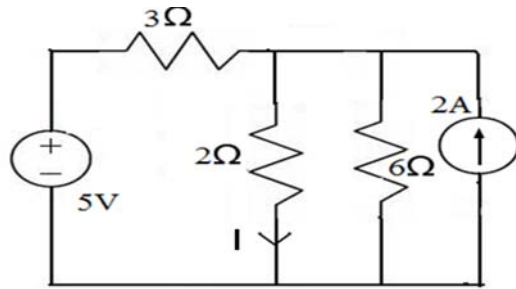પ્રશ્ન ૪ અ સુપર પોઝીસન થીયરમ નો ઉપયોગ કરી ને ૨ ઓહ્મ અવરોધ માથી પસાર થતો વિદ્યુત પ્રવાહ શોધો. 07




બ મીલમેન અને નોર્ટન થીયરમ ટુંક મા વર્ણવો.

પ્રશ્ન ૫ અ ટુ- પોર્ટ નેટવર્ક માટે ઓપન સર્કીટ ઈમ્પીડંસ ની ગણતરી કરો.

07

બ આપેલ સર્કીટ માટે Y- પેરામીટર ની ગણતરી કરો.

07

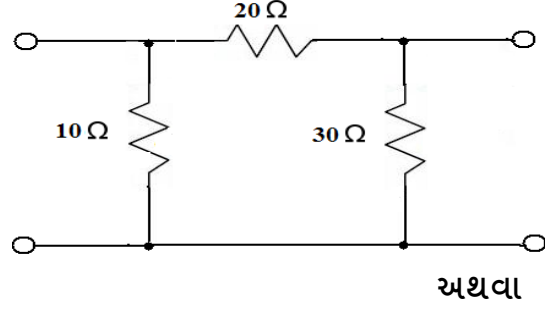

પ્રશ્ન ૫ અ સર્કિટ એલીમેન્ટ - રસીસ્ટર કેપેસીટર અને ઇન્ડક્ટર ની ઇનીસીયલ કન્ડીશન લખો.

07

બ ડી.સી. વોલ્ટેજ સોર્સ સાથે જોડાયેલી સીરીઝ R-C સર્કીટ માટે નુ ટાઈમ રીસ્પોન્સ સમીકરણ તારવો.

07
