

GUJARAT TECHNOLOGICAL UNIVERSITY**DIPLOMA ENGINEERING - SEMESTER-V • EXAMINATION – SUMMER 2013****Subject Code: 352401****Date: 10-05-2013****Subject Name: Electrical Drives and Control-I****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- | | | |
|------------|--|-----------|
| Q.1 | (a) List advantages of Electrical drive and Draw & compare torque-speed characteristic of DC Shunt/Series/Compound Motor. | 07 |
| | (b) Explain Ward-Leonard method along with circuit diagram, advantages, disadvantage and applications. | 07 |
| Q.2 | (a) Explain 1-phase half wave controlled DC drive (without freewheeling diode) along with various waveforms. | 07 |
| | (b) Draw basic block diagram of electric drive and explain each block in brief. | 07 |
| OR | | |
| | (b) Explain stepper motor drives. | 07 |
| Q.3 | (a) Draw circuit diagram and various waveforms for 1- Φ full-converter with separately excited DC motor. | 07 |
| | (b) For a 1- Φ half controlled converter of separately excited DC motor for continuous conduction derive output voltage and speed equation. | 07 |
| OR | | |
| Q.3 | (a) Draw circuit diagram and various waveforms for 1- Φ semi-converter with separately excited DC motor. | 07 |
| | (b) Explain 1- Φ half-converter (without freewheeling diode) with separately excited DC motor along with circuit diagram and various waveforms. | 07 |
| Q.4 | (a) Explain PLL control. | 07 |
| | (b) Draw circuit diagram and waveforms for 3-phase Half controlled DC drive. | 07 |
| OR | | |
| Q.4 | (a) Explain close loop control drive (any) with suitable applications. | 07 |
| | (b) For the power factor improvement discuss phase angle control method with suitable 1-phase DC drive. | 07 |
| Q.5 | (a) Explain 1-phase full controlled dual converter supporting circuit diagram and waveforms in brief. | 07 |
| | (b) List various braking and explain regenerative braking. | 07 |
| OR | | |
| Q.5 | (a) Write short note on Permanent magnet Brushless DC Motor Drives. | 07 |
| | (b) What are the adverse effects of heating in electric Motor? Discuss about load diagram, duty cycle and overload capacity of Motor. | 07 |

સૂચના:

1. તમામ પાંચ પ્રશ્નોના જવાબ ફરજીયાત છે.
2. જરૂર જણાય ત્યાં યથાયોગ્ય ધારણાઓ બાંધવી.
3. જમણી બાજુ દશમ્ભેલ આંકડા પ્રશ્નોના પૂરા ગુણ દશમ્ભે છે.
4. અંગ્રેજી પત્ર આધારભૂત ગણાશે.

પ્રશ્ન-૧	અ ઇલેક્ટ્રિકલ ડ્રાઇવ ના ફાયદા ઓ ની યાદી બનાવોઅને ડીસી શંટ/સીરીજ/કમ્પાઉન્ડ મોટર ની ટોર્ક-સ્પીડ કેરેક્ટરીસ્ટીક દોરો. 07
	બ વાઈ-લિયોનાઈ સિસ્ટમ માટે બેજિક સ્કિમેટિક ડાયાગ્રામ, ફાયદા, ગેર-ફાયદા અને યોગ્ય ઉદાહરણ સાથે દોરો અને વર્ણન કરો. 07
પ્રશ્ન-૨	અ 1-ફેઝ હાફ-વેવ કંટ્રોલ્સ ડિસિ ડ્રાઇવ (ફીલ્ડલિંગ ડાયોડ વગર) નુ જુદા-જુદા વેવફોર્મ સાથે વર્ણન કરો. 07
	બ ઇલેક્ટ્રિક ડ્રાઇવ નો બેસીક બ્લોક ડાયાગ્રામ દોરો અને દરેક બ્લોક નુ ટુક મા વર્ણન કરો. 07
અથવા	
	બ સ્ટેપર મોટર ડ્રાઇવ નુ વર્ણન કરો. 07
પ્રશ્ન-૩	અ 1-ફેઝ ફુલ-કંવર્ટર સેપરેટલી એકસાઇટેડ ડિસિ મોટર ની સર્કિટ અને જુદા-જુદા વેવફોર્મ દોરો. 07
	બ 1-ફેઝ ફુલ વેવ કંટ્રોલર કનેક્ટેડ વીથ 1-ફેઝ સેપરેટલી એકસાઇટેડ ડિસિ મોટર ના કંટીન્યુઅસ કરંટ મોડ માટે આઉટપુટ વોલ્ટેજ અને સ્પીડ ના સુત્રો તાર્વો. 07
અથવા	
પ્રશ્ન-૩	અ 1-ફેઝ સેમી-કંવર્ટર સેપરેટલી એકસાઇટેડ ડિસિ મોટર ની સર્કિટ અને જુદા-જુદા વેવફોર્મ દોરો. 07
	બ 1-ફેઝ હાફ-કંવર્ટર (ફીલ્ડલિંગ ડાયોડ વગર)સેપરેટલી એકસાઇટેડ ડિસિ મોટર ની સર્કિટ અને જુદા-જુદા વેવફોર્મ સાથે વર્ણન કરો. 07
પ્રશ્ન-૪	અ PLL Control નુ વર્ણન કરો. 07
	બ ૩-ફેઝ હાફ કંટ્રોલ્સ ડિસિ ડ્રાઇવ નિ સર્કિટ અને વેવ-ફોર્મ દોરો. 07
અથવા	
પ્રશ્ન-૪	અ યોગ્ય ઉપયોગિતા સાથે ક્લોજ લૂપ ડ્રાઇવ(કોઇપણ)નુ વર્ણન કરો. 07
	બ પાવર ફેક્ટર ના સુધારા માટે યોગ્ય 1-ફેઝ ડિસિ ડ્રાઇવ માટે ફેઝ એંગલ કંટ્રોલ પદ્ધતિ દ્વારા સમજાવો. 07
પ્રશ્ન-૫	અ 1-ફેઝ ફુલ કંટ્રોલ્સ ડુઅલ કંવર્ટર ને સર્કિટ ડાયાગ્રામ અને વેવ-ફોર્મ સાથે ટુક મા વર્ણન કરો. 07
	બ જુદા-જુદા ઇલેક્ટ્રિક બ્રેકિંગ નુ લિસ્ટ બનાવો અનેરીજનરેટીવ બ્રેકિંગ નુ વર્ણન કરો 07

અથવા

- પ્રશ્ન-૫ અ પરમેનંટ મેઝનેટ બ્રશલેશ ડિસિ મોટર ડ્રાઇવ પર ટુંકનોંધ લખો. 07
- બ હિટિંગ નિ ઇલેક્ટ્રિક મોટર મા ખરાબ અસર શું છે? લોડ ડાયાગ્રામ, 07
- ડ્યુટી સાયકલ અને ઓવર લોડ કેપેસિટી વિષે ચર્ચા કરો.
