

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-V • EXAMINATION – SUMMER 2013****Subject Code: 352403****Date: 16-05-2013****Subject Name: Power Electronics Circuits****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Define and classify Rectifiers. Draw circuit diagram with waveform of half controlled converter for RC load. **07**
- (b) Draw circuit diagram and waveform of Single phase parallel dual converter. **07**
- Q.2** (a) Draw circuit diagram and waveform of Three phase uncontrolled converter. Explain it. **07**
- (b) Draw circuit diagram and waveform of full controlled bridge converter with R-L load. Explain it. **07**
- OR**
- (b) Draw Ac regulators with pure inductors and explain it. **07**
- Q.3** (a) Draw Buck (step-down) converter explain it with Steady-state and Continuous Current Mode operation. Explain it. **07**
- (b) Give Basic Block diagram of SMPS. Explain it. **07**
- OR**
- Q.3** (a) Explain Buck-Boost converter with waveform. Obtain output voltage equation for steady state operation. **07**
- (b) Write a short note on AC chopper Regulator. **07**
- Q.4** (a) Explain High frequency transformer. Explain Flyback Converter with waveform. **07**
- (b) Explain voltage (impulse) commutation of chopper with necessary diagram and waveform. **07**
- OR**
- Q.4** (a) Explain Harmonics Filtering in Inverter. **07**
- (b) Explain Single phase half bridge voltage source inverters with RL and RC load. **07**
- Q.5** (a) Write a short note on ZVS resonant switch converter. **07**
- (b) Write a short note on resonant DC link converter. **07**
- OR**
- Q.5** (a) Draw various schemes used for inverter voltage control by control of DC input voltage. **07**
- (b) Draw and explain Three Phase current source inverter. **07**

પ્રશ્ન-૧	અ	રેક્ટીફાયર વ્યાખ્યાતીત કરી વર્ગીકરણ કરો. RC લોડ માટે હાફ કંટ્રોલ કન્વર્ટર પરીપથ વેવફોર્મ સાથે દોરો.	૦૭
	બ	સિંગલ ફેઝ સમાંતર ડ્યુઅલ કન્વર્ટર માટે પરીપથ વેવફોર્મ સાથે દોરો.	૦૭
પ્રશ્ન-૨	અ	ત્રણ ફેઝ અન કંટ્રોલ કન્વર્ટર માટે પરીપથ વેવફોર્મ સાથે દોરી સમજાવો.	૦૭
	બ	કુલ કંટ્રોલ બીજ કન્વર્ટર RL લોડ માટે પરીપથ વેવફોર્મ સાથે દોરી સમજાવો.	૦૭
અથવા			
પ્રશ્ન-૩	અ	બક કન્વર્ટર દોરો. સ્ટેડી સ્ટેટ કંટીન્યુસ કરંટ મોડ સમજાવો.	૦૭
	બ	SMPS નો બ્લોક પરીપથ દોરી સમજાવો.	૦૭
અથવા			
પ્રશ્ન-૩	અ	બક બુસ્ટ કન્વર્ટર વેવફોર્મ દોરો. આઉટ પુટ વોલ્ટેજ સુત્ર મેળવો.	૦૭
	બ	એ. સી ચોપર રેગ્યુલેટર માટે ટુંકમાં લખો.	૦૭
પ્રશ્ન-૪	અ	હાઈ ફ્રીક્વેન્સી ટ્રાંસફોર્મર સમજાવો. ફ્લાય બેક કન્વર્ટર વેવફોર્મ સાથે દોરી સમજાવો.	૦૭
	બ	વોલ્ટેજ કોમ્યુટેસન ચોપર પરીપથ વેવફોર્મ સાથે દોરી સમજાવો.	૦૭
અથવા			
પ્રશ્ન-૪	અ	ઈંવર્ટર માટે હારમોનિક ફીલ્ટરીંગ સમજાવો.	૦૭
	બ	સિંગલ ફેઝ હાફ બીજ વોલ્ટેજ સોર્સ ઈંવર્ટર RL અને RC લોડ માટે સમજાવો.	૦૭
પ્રશ્ન-૫	અ	ZVS રેસોનન્ટ સ્વીચ કન્વર્ટર માટે ટુંકમાં લખો.	૦૭
	બ	રેસોનન્ટ ડી.સી. લીફ કન્વર્ટર માટે ટુંકમાં લખો.	૦૭
અથવા			
પ્રશ્ન-૫	અ	ડી.સી. ઈંનપુટ વોલ્ટેજ કંટ્રોલની મદદથી ઈંવર્ટર વોલ્ટેજ કંટ્રોલ કરવાની પદ્ધતી દોરી સમજાવો.	૦૭
	બ	ત્રણ ફેઝ ફરંટ સોર્સ ઈંવર્ટર દોરી સમજાવો.	૦૭
