

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-VI • EXAMINATION – SUMMER 2013****Subject Code: 361702****Date: 13/05/2013****Subject Name: Industrial Electronics and Control****Time: 10:30 am TO 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Draw and explain SCR snubber circuit. **07**
(b) State various methods of commutation. Describe class-C commutation with help circuit diagram & wave form. **07**
- Q.2** (a) Explain construction ,working & characteristics of DIAC with neat sketch. **07**
(b) With diagram define (1) Latching current (2) Holding current (3) Turn on time (4) Turn off time, for SCR **07**
- OR**
- (b) Define various properties of UJT. **07**
- Q.3** (a) Explain operation of full controlled converter with resistive load. **07**
(b) Explain operation of cyclo-converter with resistive load. **07**
- OR**
- Q.3** (a) What is dual converter ? Discuss it. State its merit & demerit. **07**
(b) Explain application , merit & demerit of cyclo-converter. **07**
- Q.4** (a) What is chopper ? Discuss operation of chopper for capacitive load. **07**
(b) Explain dc motor speed control using field current control. **07**
- OR**
- Q.4** (a) Discuss operation of parallel inverter. **07**
(b) List turn on methods of SCR. Explain one of them. **07**
- Q.5** (a) Which are different methods for speed control of ac motor. Explain rotor resistance control method. **07**
(b) Explain dc motor speed control using armature voltage control. **07**
- OR**
- Q.5** (a) Explain stator voltage control for ac motor.. **07**
(b) Explain working of capacitor energy storage welding ,write its Application. **07**

પ્રશ્ન-૧	અ	એસ.સી.આર. સ્વભર પરિપથ દોરો અને સમજાવો.	૦૭
	બ	COMMUTATION ની વિવિધ પદ્ધતિ લખો અને CLASS – C COMMUTATION વેવ ફોર્મ અને વર્કિંગ આકૃતિ દોરી સમજાવો.	૦૭
પ્રશ્ન-૨	અ	DIAC નું કંસ્ટ્રક્શન લાક્ષણિકતા અને વર્કિંગ આકૃતિ દોરી સમજાવો.	૦૭
	બ	વ્યાખ્યા આપો (1) લેચિંગ પ્રવાહ (2) હોલ્ડિંગ પ્રવાહ (3) ટર્ન ઓન સમય (4) ટર્ન ઓફ સમય	૦૭
		અથવા	
	બ	UJT ની વિવિધ પ્રોપર્ટીઝની વ્યાખ્યા લખો.	૦૭
પ્રશ્ન-૩	અ	રેસિસ્ટીવ લોડ સાથે FULL CONTROLLED CONVERTER નું ઓપરેશન સમજાવો.	૦૭
	બ	રેસિસ્ટીવ લોડ સાથે CYCLO-CONVERTER ઓપરેશન સમજાવો.	૦૭
		અથવા	
પ્રશ્ન-૩	અ	DUAL CONVERTER એટલે શું ? તેની ચર્ચા કરો. તેના ફાયદા અને ગેર-ફાયદા કહો.	૦૭
	બ	CYCLO-CONVERTER ની ઉપયોગીતા, ફાયદા અને ગેર-ફાયદા કહો.	૦૭
પ્રશ્ન-૪	અ	CHOPPER એટલે શું? કેપેસિટીવ લોડ માટે તેના ઓપરેશનની ચર્ચા કરો.	૦૭
	બ	DC MOTOR ની SPEED CONTROL ફીલ્ડક્રંટ CONTROL થી સમજાવો.	૦૭
		અથવા	
પ્રશ્ન-૪	અ	PARALLEL INVERTER ના ઓપરેશનની ચર્ચા કરો.	૦૭
	બ	SCR ની TURN ON રીતો જણાવો અને ગમે તે એક રીત સમજાવો.	૦૭
પ્રશ્ન-૫	અ	AC MOTOR ની SPEED CONTROL ની જુદી જુદી રીતો જણાવો. અને ROTOR RESISTANCE થી SPEED CONTROL સમજાવો.	૦૭
	બ	DC MOTOR ની SPEED CONTROL આર્મેચર વોલ્ટેજ CONTROL થી સમજાવો.	૦૭
		અથવા	
પ્રશ્ન-૫	અ	એ.સી મોટરની STATOR VOLTAGE CONTROL METHOD સમજાવો.	૦૭
	બ	કેપેસિટર એનર્જી સ્ટોરેજ વેલ્ડિંગની આકૃતિ દોરી સમજાવો અને તેની ઉપયોગીતા લખો	૦૭
